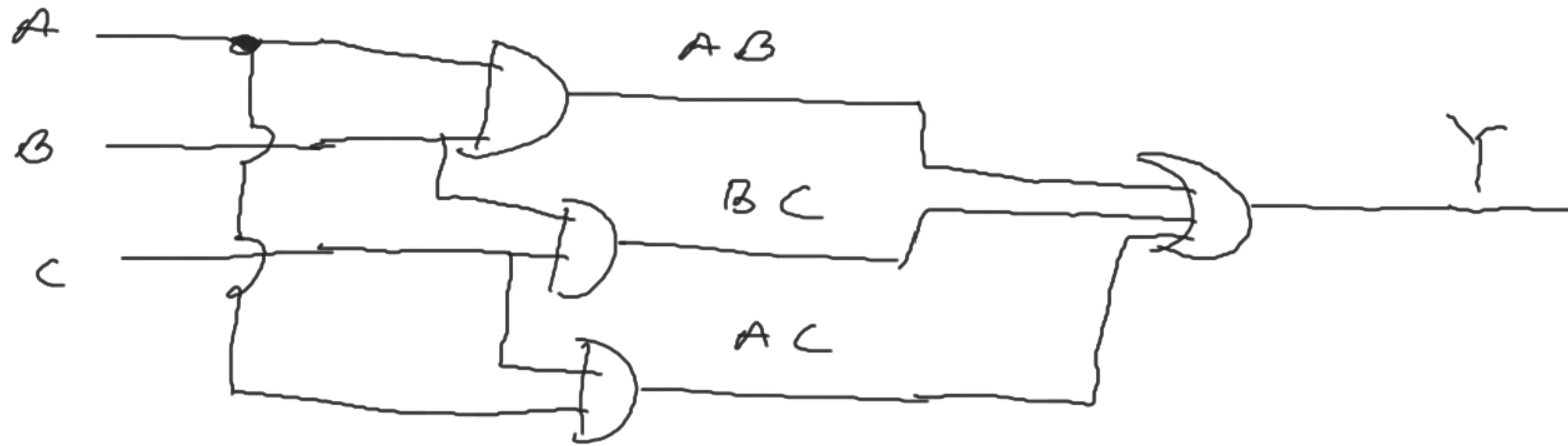


$$y = AB + BC + AC$$



Ex-OR gate:

A	B	Y
0	0	0
0	1	1 ✓
1	0	1 ✓
1	1	0

$$Y = \bar{A}B + A\bar{B}$$

$$Y = A \oplus B$$

$A \oplus B = \bar{A}B + A\bar{B}$

→ Save 4 logic gates

Ex-NOR gate:

A	B	Y
0	0	1 ✓
0	1	0
1	0	0
1	1	1 ✓

$$Y = \bar{A}\bar{B} + AB$$

$$Y = A \oplus B$$

$A \oplus B = AB + \bar{A}\bar{B}$


→ Save 4 logic gates

Design the logic circuit from the given statements.

- 1) Design a logic circuit where, There are 3 inputs A, B, C and output Y; output will be HIGH only when the majority of inputs are HIGH.

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1 ✓
1	0	0	0
1	0	1	1 —
1	1	0	1 ✓
1	1	1	1 —

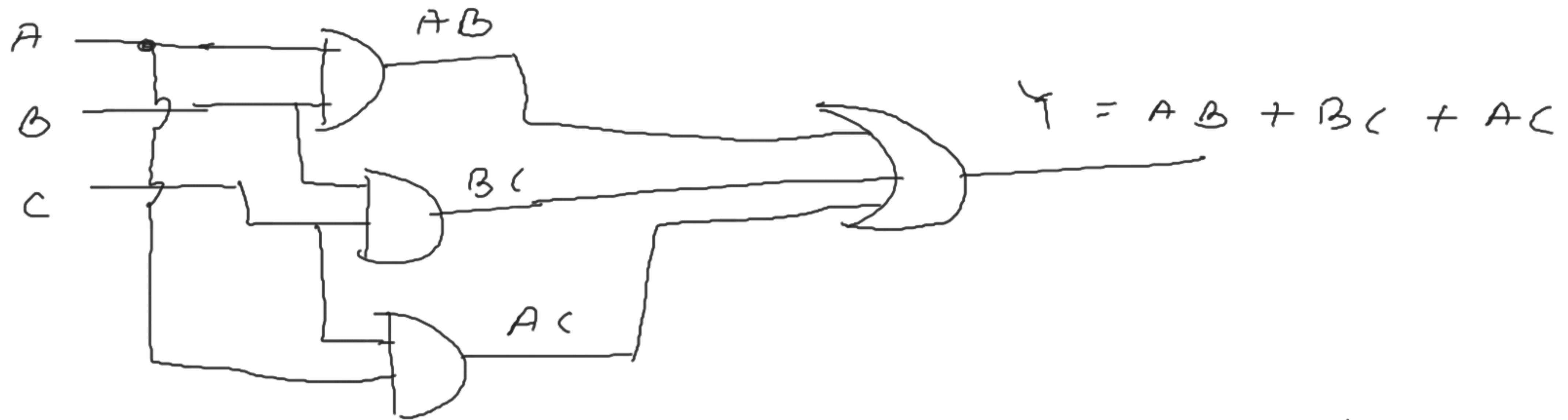
$$\begin{aligned} Y &= \bar{A}Bc + A\bar{B}c + \underline{AB\bar{C}} + ABC \\ &= \bar{A}Bc + A\bar{B}c + AB \\ &= \bar{A}Bc + A(B + \bar{B}c) \\ &= \bar{A}Bc + A(B + c) \\ &= \bar{A}Bc + AB + Ac \\ &= B(A + \bar{A}c) + Ac \\ &= B(A + c) + Ac \\ &= AB + BC + AC \end{aligned}$$



2) A, B, C are inputs and Y is output.
 Output Y will be HIGH only when
 majority of inputs are LOW. Design
 the circuit.

A	B	C	Y
0	0	0	1 ✓
0	0	1	1 ✓
0	1	0	1 ✓
0	1	1	0
1	0	0	1 ✓
1	0	1	0
1	1	0	0
1	1	1	0

$$\begin{aligned}
 Y &= \overline{\overline{A} \overline{B} \overline{C}} + \overline{\overline{A} \overline{B} C} + \overline{A} \overline{B} \overline{C} + A \overline{B} \overline{C} \\
 &= \overline{\overline{A} \overline{B}} + \overline{\overline{A} B \overline{C}} + A \overline{B} \overline{C} \\
 &= \overline{\overline{A}} (\overline{\overline{B}} + \overline{B \overline{C}}) + A \overline{B} \overline{C} \\
 &= \overline{\overline{A}} (\overline{\overline{B}} + \overline{C}) + A \overline{B} \overline{C} \\
 &= \overline{\overline{A} \overline{B}} + \overline{\overline{A} \overline{C}} + A \overline{B} \overline{C} \\
 &= \overline{\overline{A} \overline{B}} + \overline{C} (\overline{\overline{A}} + A \overline{B}) \\
 &= \overline{\overline{A} \overline{B}} + \overline{C} (\overline{\overline{A}} + \overline{B}) \quad \cancel{+} \\
 &= \overline{\overline{A} \overline{B}} + \overline{\overline{A} \overline{C}} + \overline{\overline{B} C}
 \end{aligned}$$

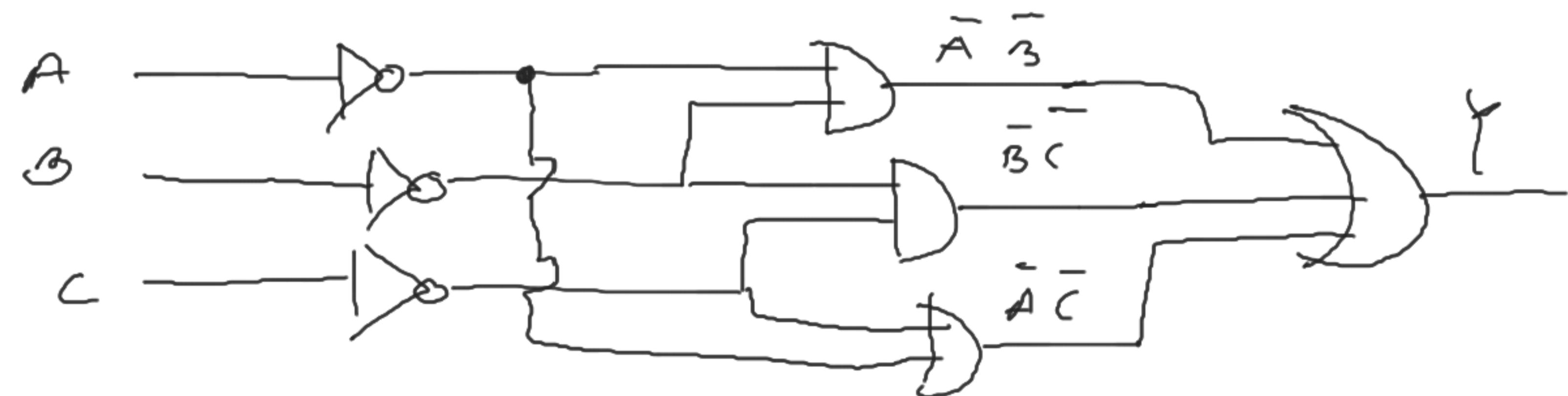

3) $A, B, C \Rightarrow \text{Inputs } X \Rightarrow \text{Output } X$

$\left\{ \begin{array}{l} X = A \rightarrow B \text{ and } C \text{ are same} \\ X = 1 \rightarrow B \text{ and } C \text{ are different} \end{array} \right.$

A	B	C	X
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$$\begin{aligned}
 X &= \bar{A}\bar{B}C + \bar{A}B\bar{C} + \underline{\bar{A}B\bar{C}} + \underline{\bar{A}\bar{B}C} \\
 &\quad + \underline{\bar{A}BC} + \underline{ABC} \\
 &= \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B} + AB \\
 &= \bar{A}\bar{B}C + \bar{A}B\bar{C} + A \\
 &= \bar{A}(\bar{B}C + B\bar{C}) + A \\
 &= A + \bar{A}(B \oplus C) \\
 X &= A + (B \oplus C)
 \end{aligned}$$

$$n + \bar{n}y = n + y$$



4)


D	C	B	A	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

$$> \begin{matrix} 0 & 0 & 1 & 0 & 2 \\ \hline 3 & \leq & Y & \leq & 9 \end{matrix} \quad < 1 & 0 & 1 & 0 & 2$$

$$n + \bar{n}y = n + y$$

$$\begin{aligned}
Y &= AB\bar{C}\bar{D} + \boxed{\bar{A}\bar{B}C\bar{D} + A\bar{B}C\bar{D}} + \bar{A}\bar{B}CD \\
&\quad + \bar{ABC}\bar{D} + \boxed{\bar{A}\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}\bar{D}} \\
&= AB\bar{C}\bar{D} + \bar{B}\bar{C}\bar{D}(\bar{A} + A) + BC\bar{D}(\bar{A} + A) + \bar{B}\bar{C}\bar{D}(\bar{A} + A) \\
&= AB\bar{C}\bar{D} + \boxed{\bar{B}\bar{C}\bar{D} + BC\bar{D}} + \bar{B}\bar{C}\bar{D} \\
&= AB\bar{C}\bar{D} + \bar{C}\bar{D}(\bar{B} + B) + \bar{B}\bar{C}\bar{D} \\
&= AB\bar{C}\bar{D} + \bar{C}\bar{D} + \bar{B}\bar{C}\bar{D} \\
&= \bar{D}(C + \bar{C}AB) + \bar{B}\bar{C}\bar{D} \\
&= \bar{D}(C + AB) + \bar{B}\bar{C}\bar{D} \\
&= \bar{C}\bar{D} + AB\bar{D} + \bar{B}\bar{C}\bar{D} \\
&= CD + AB\bar{D} + \bar{B}\bar{C}\bar{D}
\end{aligned}$$
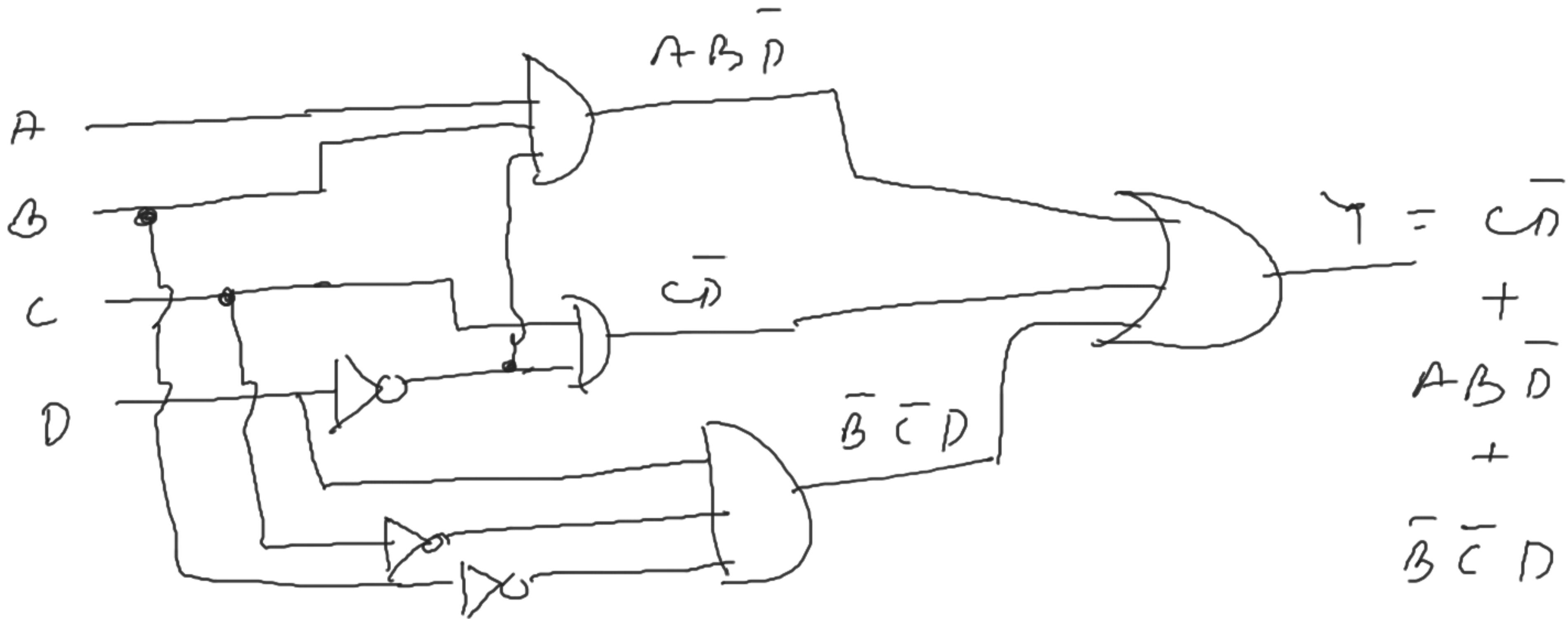
$$Y = C\bar{D} + AB\bar{D} + \bar{B}\bar{C}D$$



6) $A \ B \ C \ D \quad Y$

0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

(A is HIGH) AND (At least 2 other inputs are HIGH)

$\text{Ans} \leftarrow A \bar{B} (\bar{C} + \bar{D})$

$A \bar{C} D + A \bar{B} (\bar{C} + \bar{D})$

$Y = A \bar{B} C \bar{D} + A B \bar{C} \bar{D} + A \bar{B} C \bar{D} + A B C \bar{D}$

$= A \bar{B} C \bar{D} + A B \bar{C} \bar{D} + A B C \bar{D}$

$= A \bar{B} C \bar{D} + A B (C + \bar{C} \bar{D})$

$= A \bar{B} C \bar{D} + A B (C + D)$

$= A \bar{B} C \bar{D} + A B C + A \bar{B} D$

The $= A C (B + \bar{B} D) + A B D$





Row circuit. $= A C (B + D) + A B D$

$= A B C + A C \bar{D} + A B D$



$= A (B C + C \bar{D} + B D)$

Universality of NAND gate:


NAND \longrightarrow Basic gate

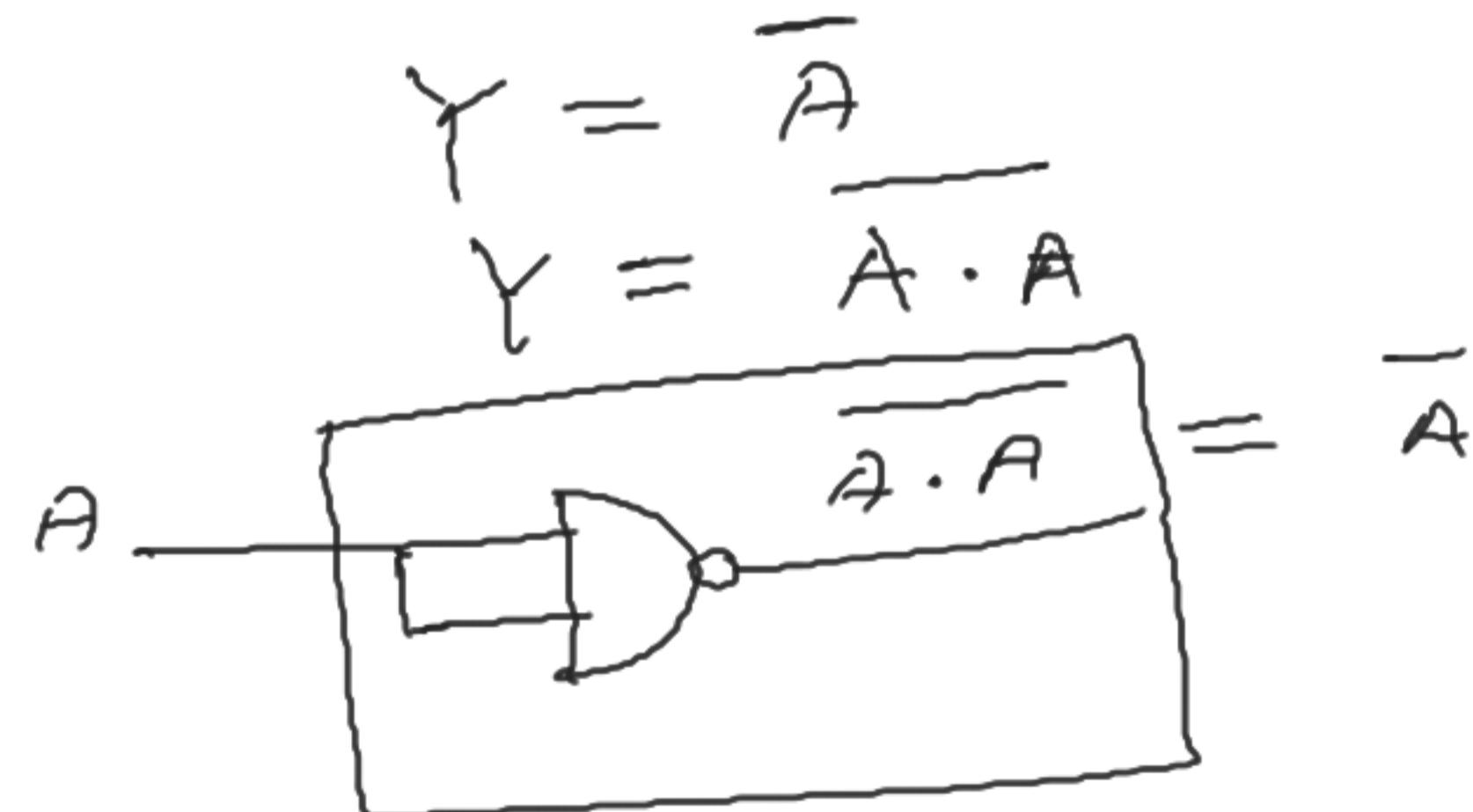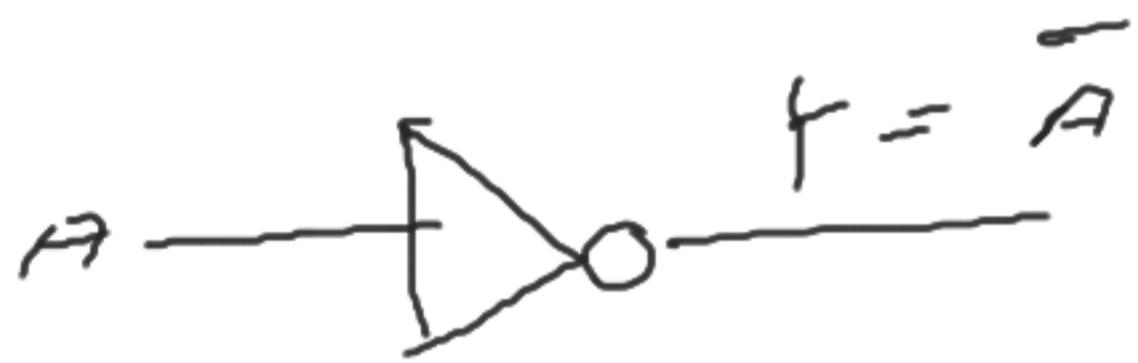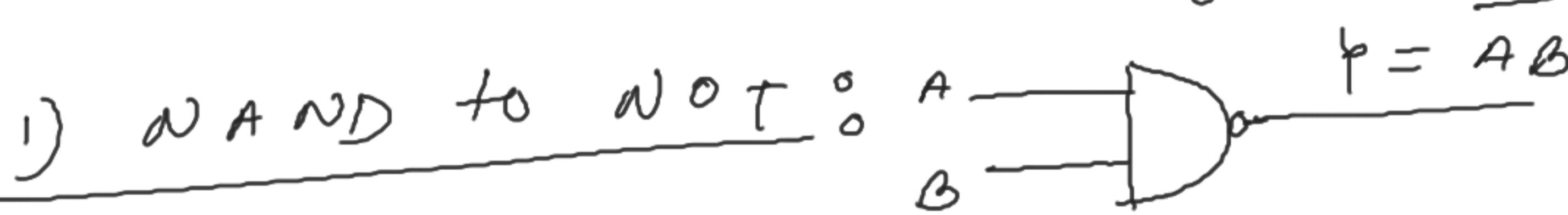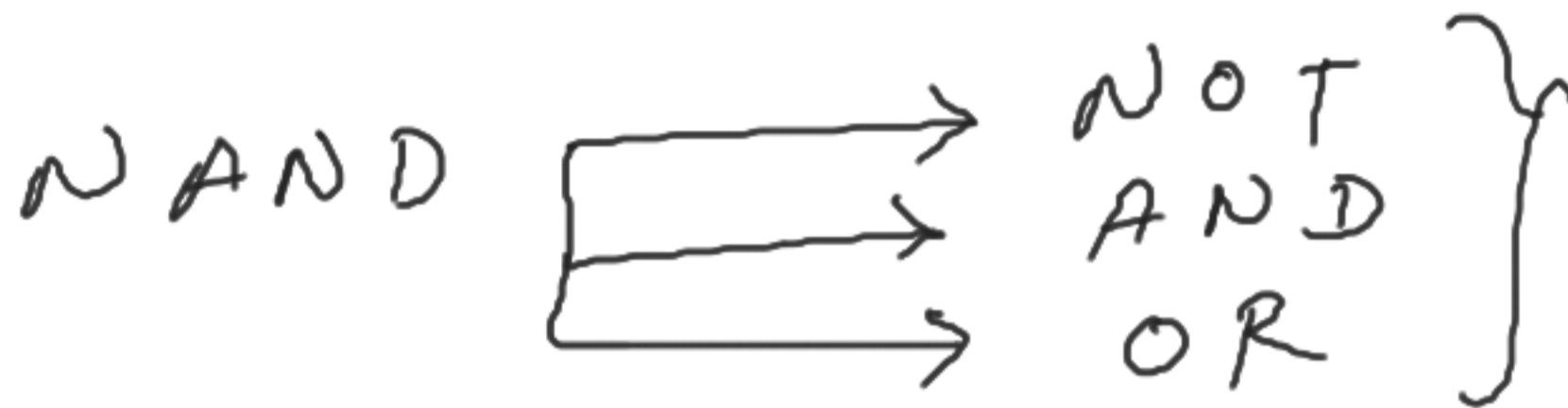

2) NAND TO AND:

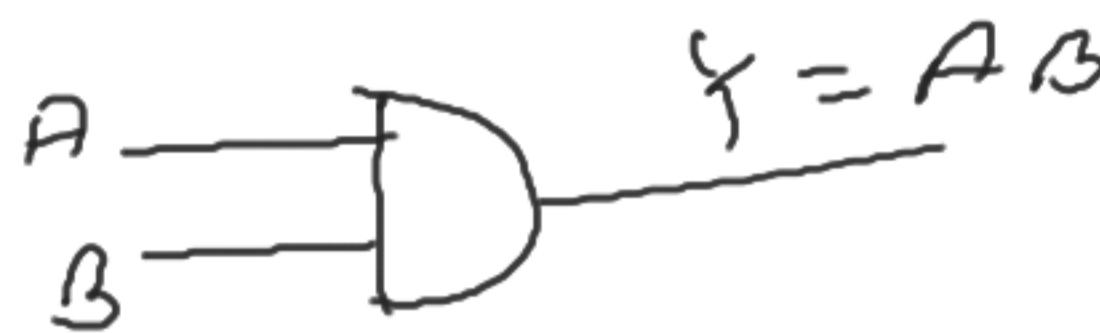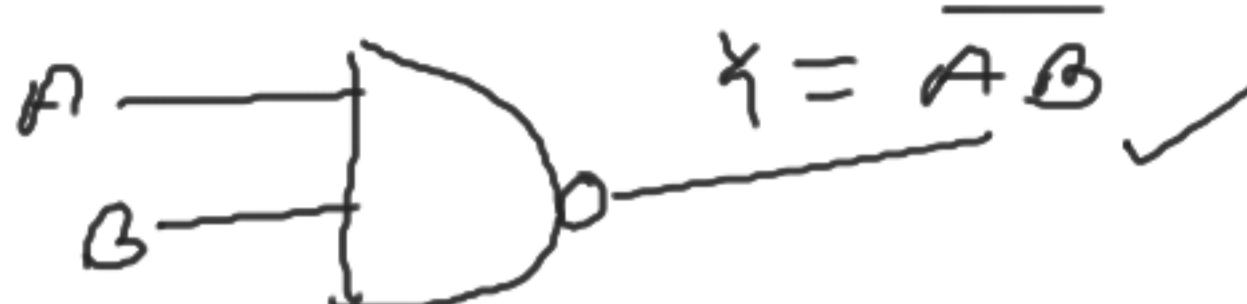


$$Y = AB = (\overline{A}\overline{B})$$

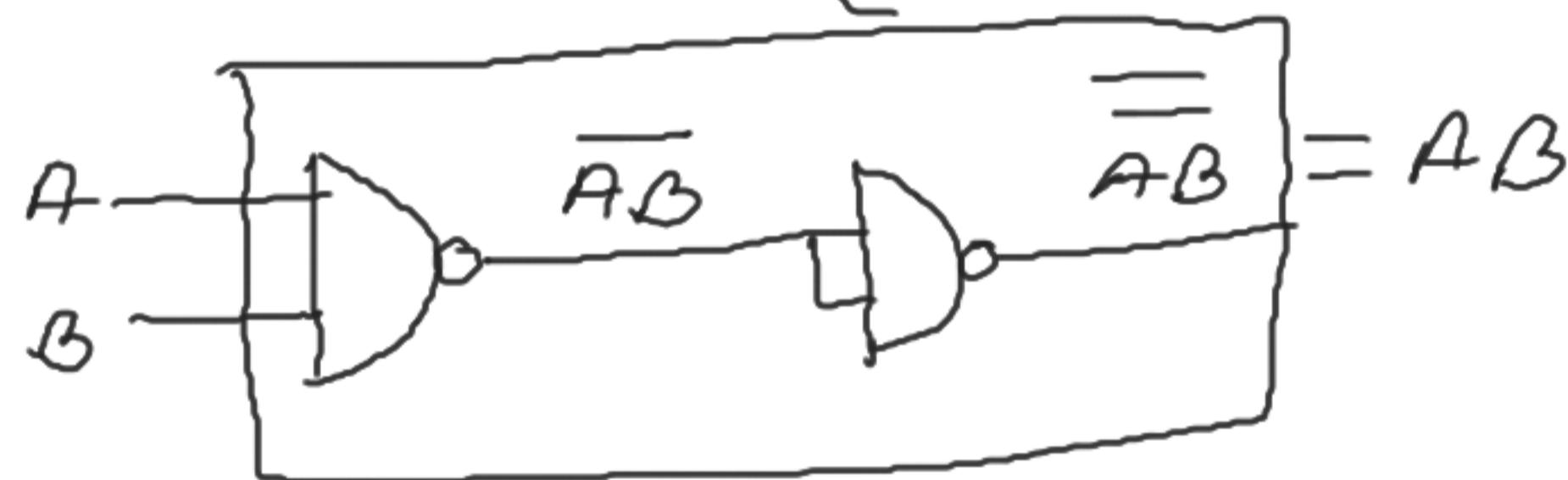

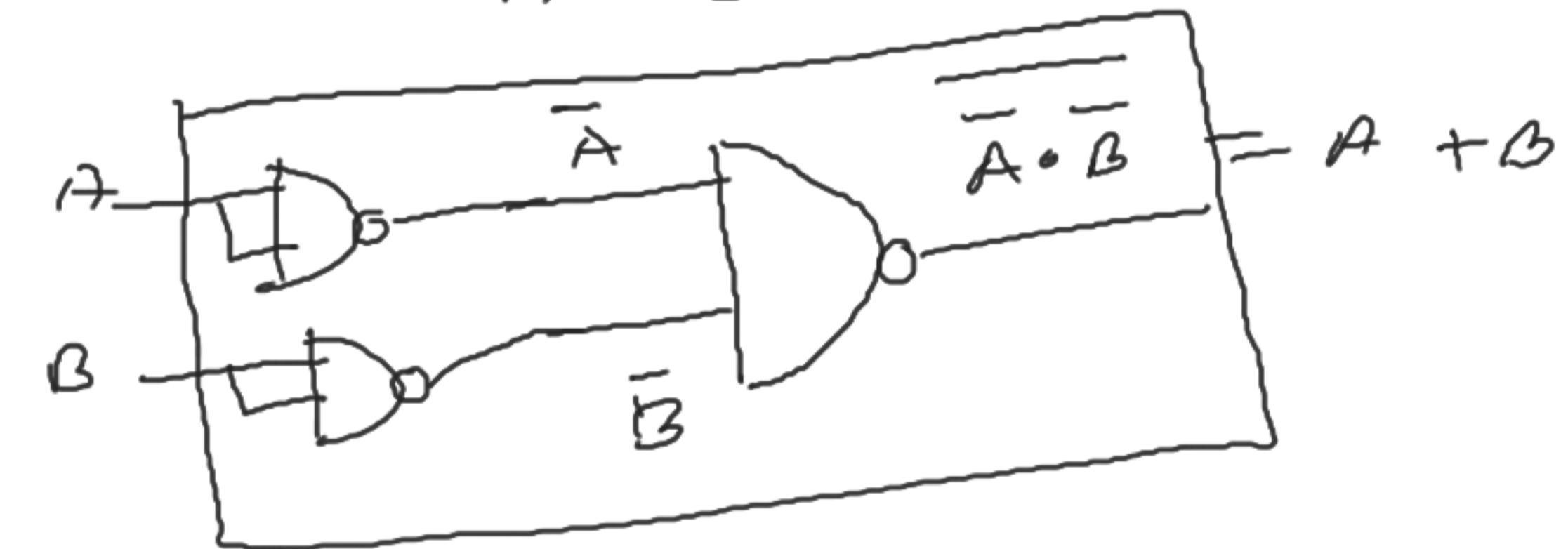
3) NAND TO OR:




$$\begin{aligned} Y &= A + B = \overline{(\overline{A} + \overline{B})} \\ &= \overline{\overline{A} \cdot \overline{B}} \end{aligned}$$



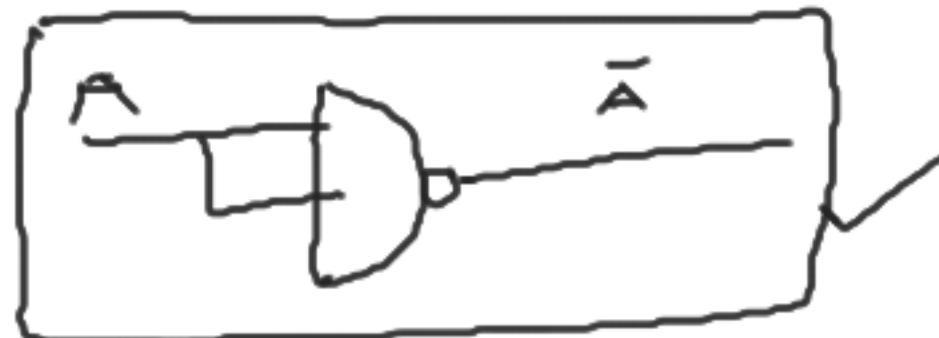
so, we can design all the basic gates using NAND gate only. Therefore NAND gate is called Universal gate.



NOT

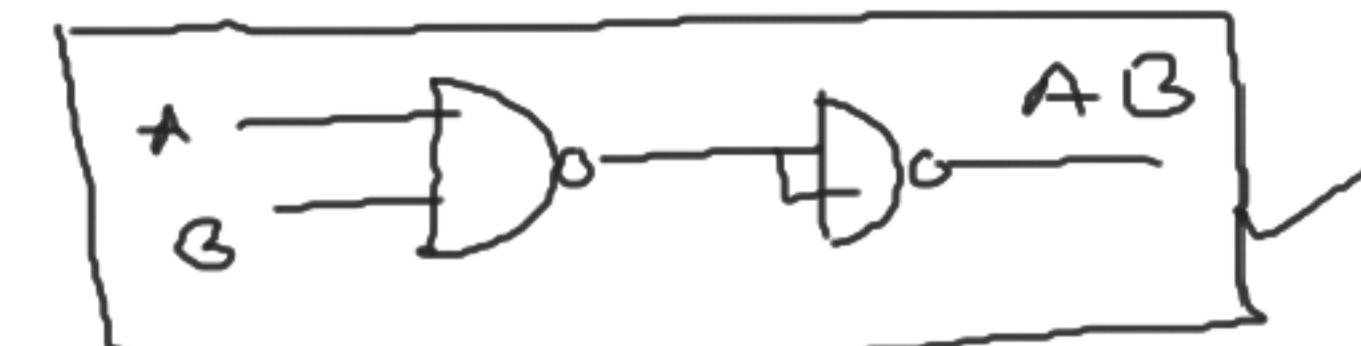


AND

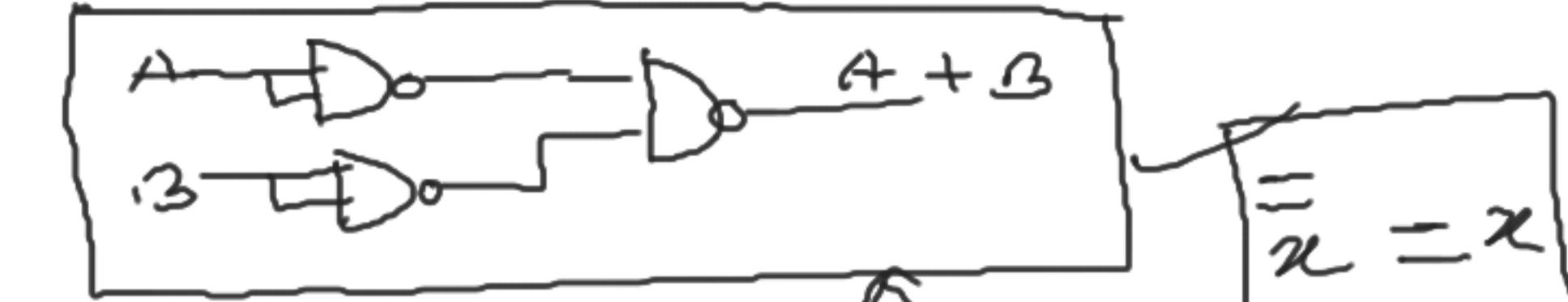

OR


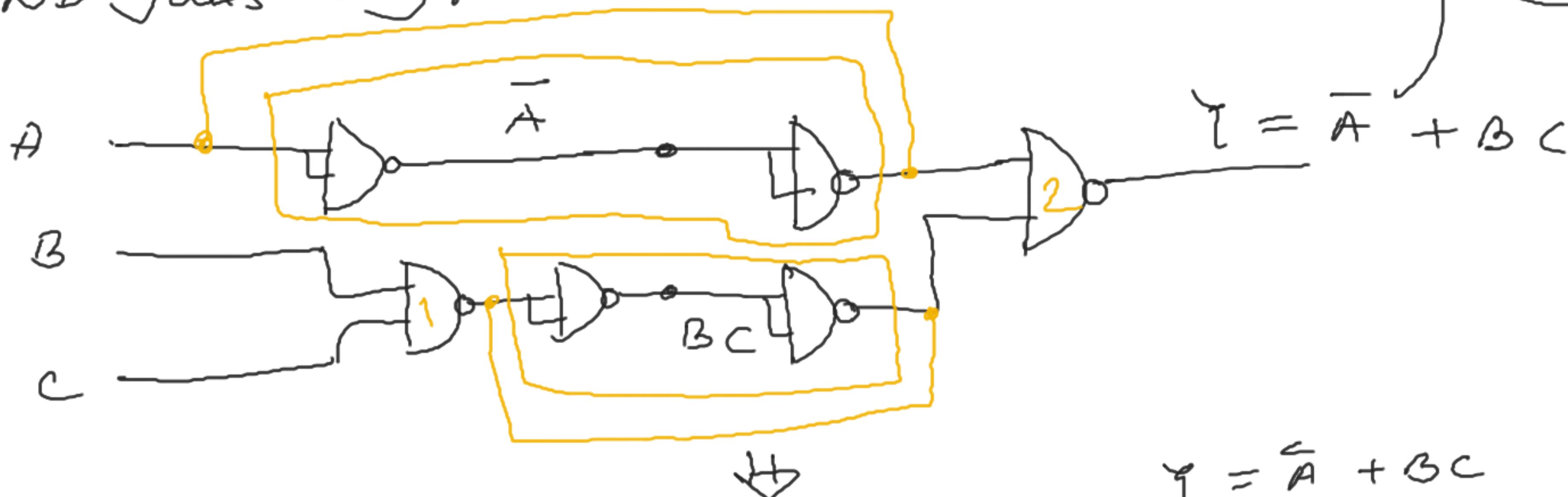
Draw the circuit diagram of $y = \bar{A} + BC$ using NAND gates only.





Draw

$$y = \overline{A}B + A\overline{B}C$$

using nAND gates only.

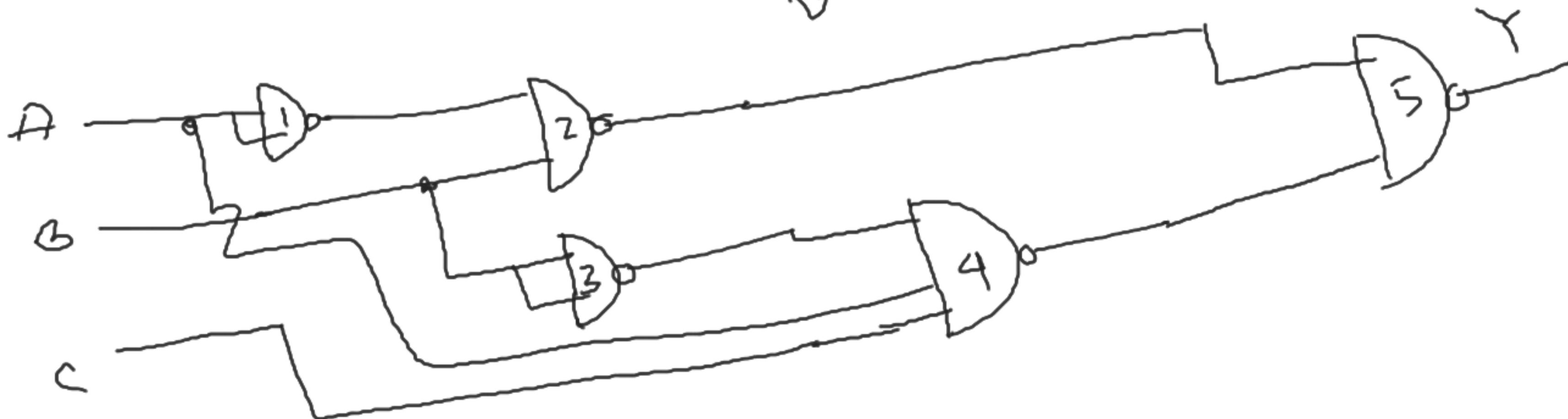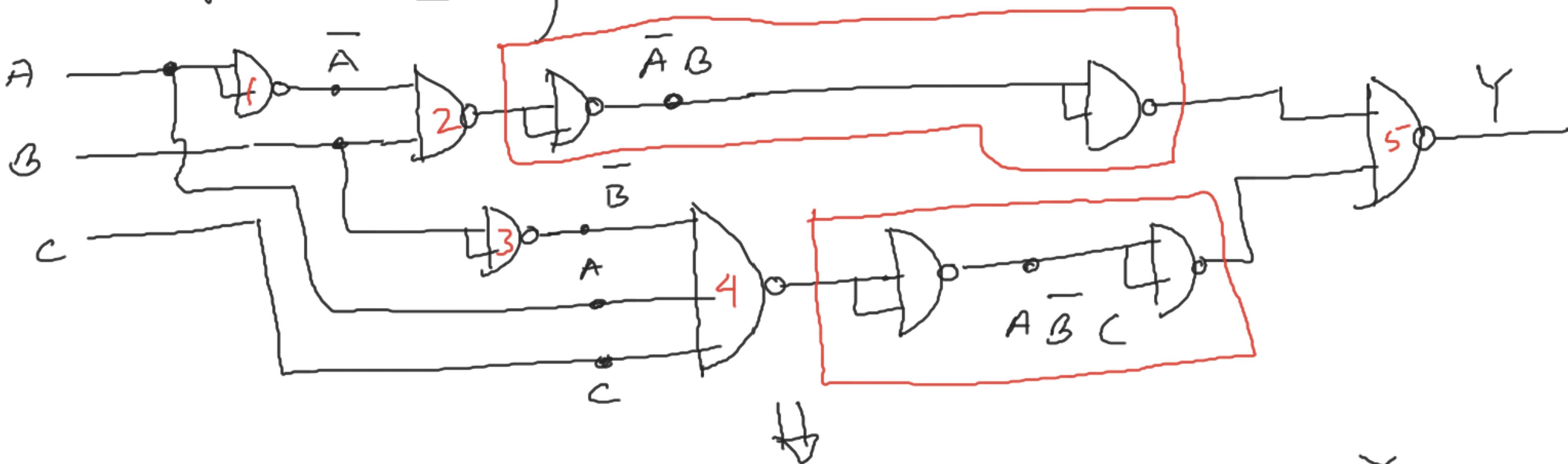

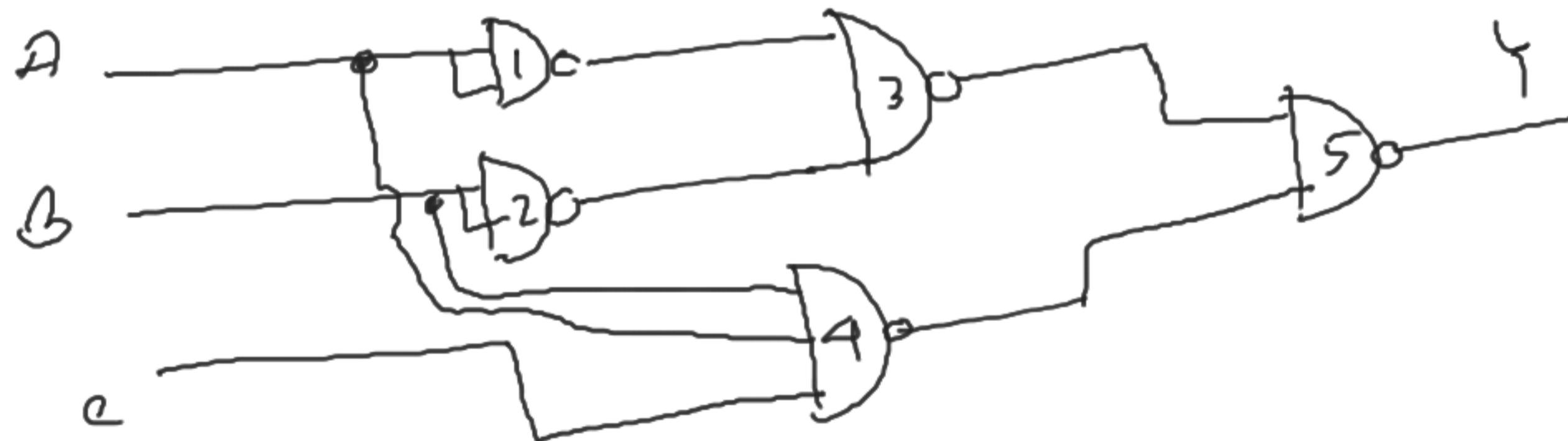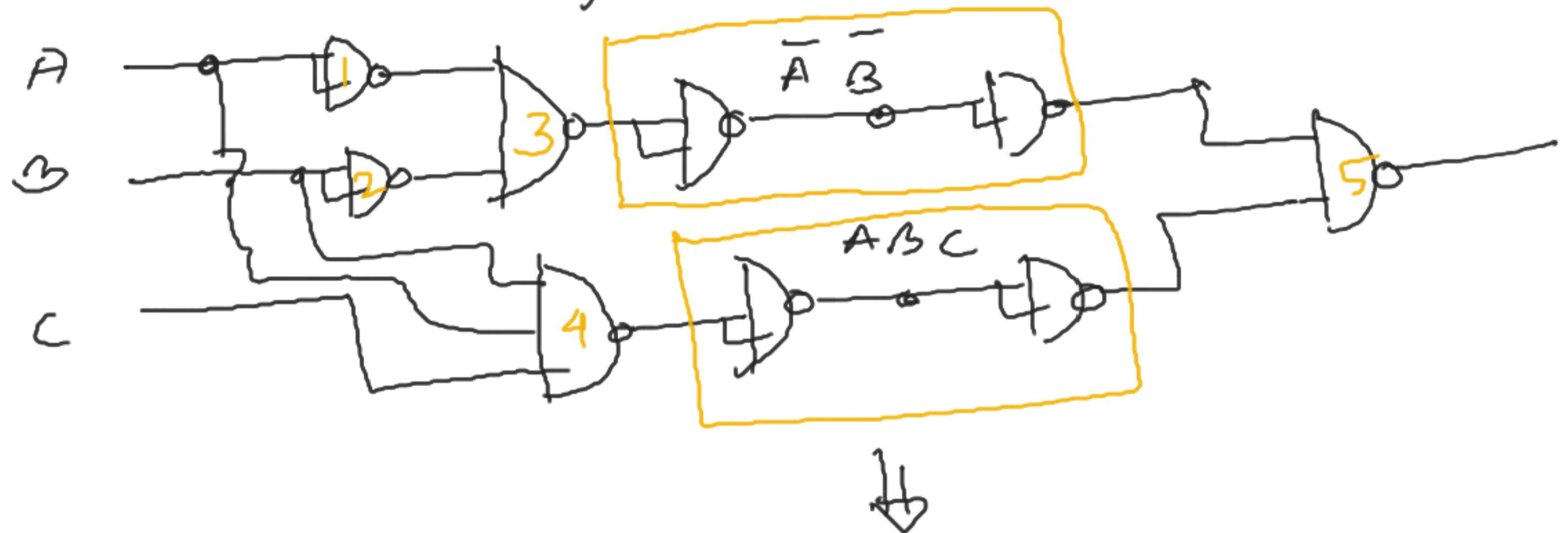Draw $y = \bar{A}\bar{B} + A\bar{B}C$ using NAND gates only.




Universality of NOR gate :





$$Y = \bar{A} + \bar{B}$$

i) NOR to NOT

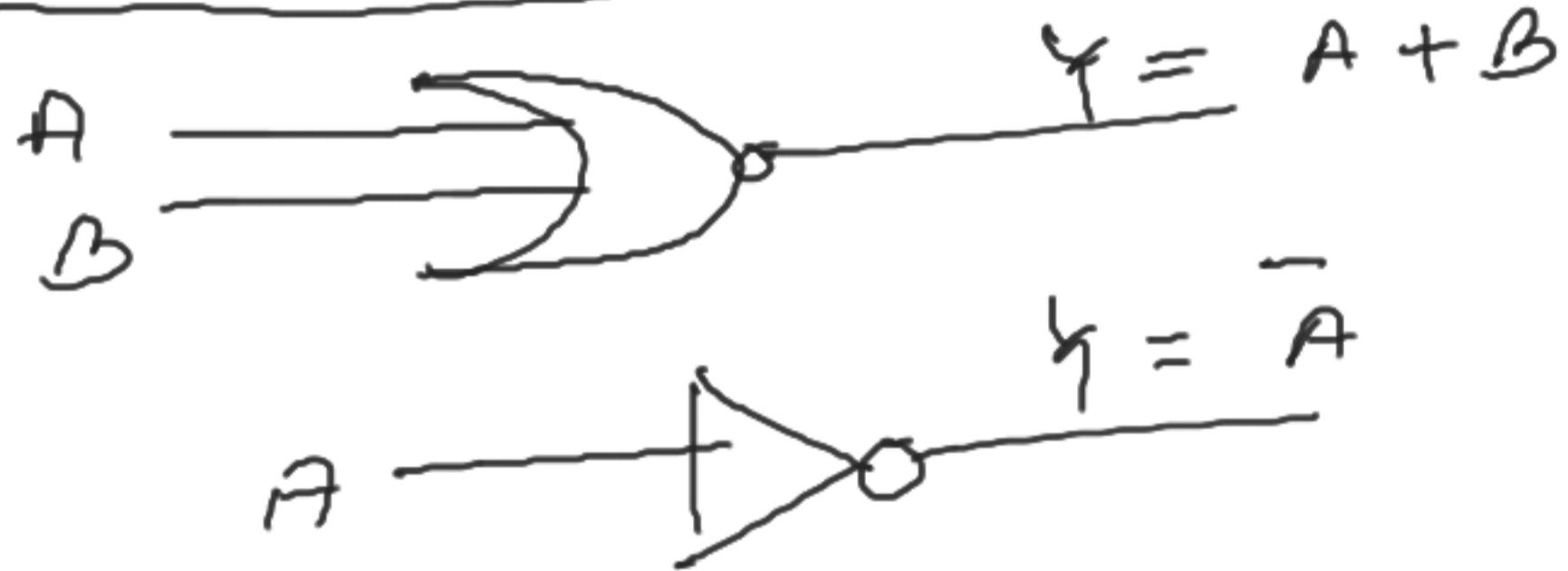


$$\begin{aligned} Y &= \bar{A} \\ &= \overline{\bar{A} + \bar{A}} \\ A &\rightarrow \boxed{\text{NOR gate}} = \bar{A} \end{aligned}$$

2) NOR to OR:

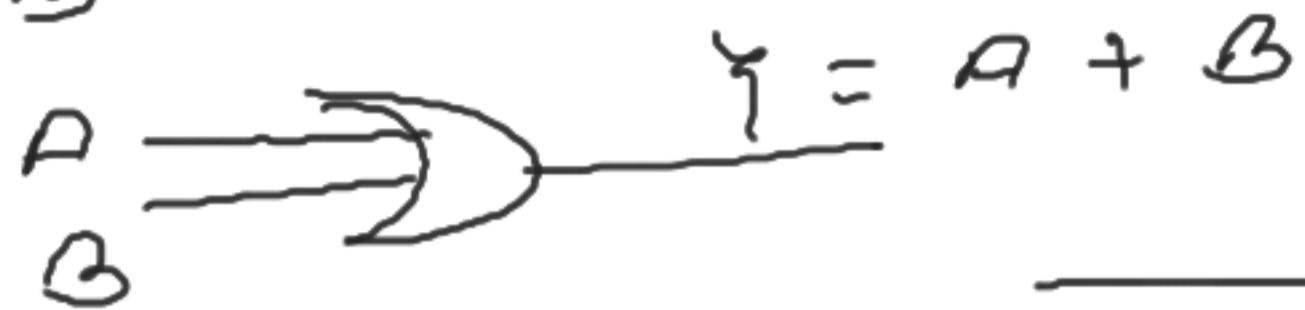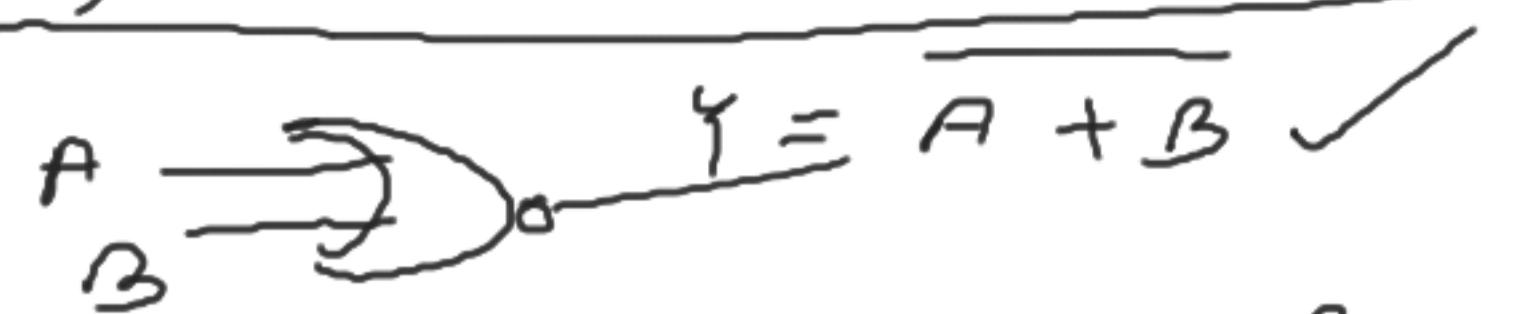

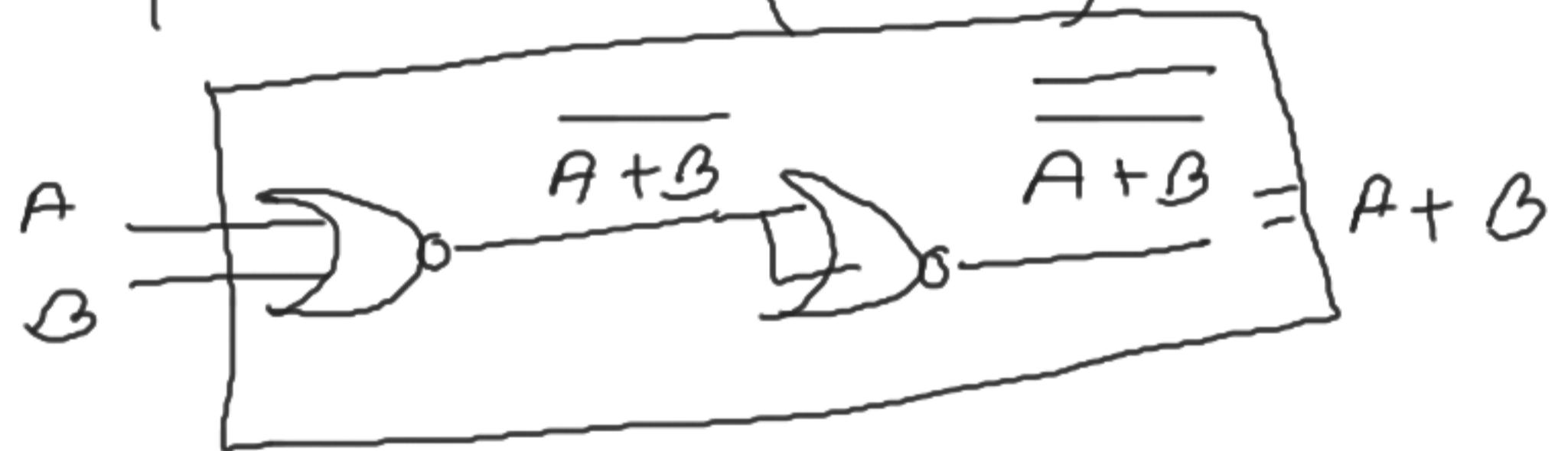
$$Y = A + B = (\overline{A} + \overline{B})$$




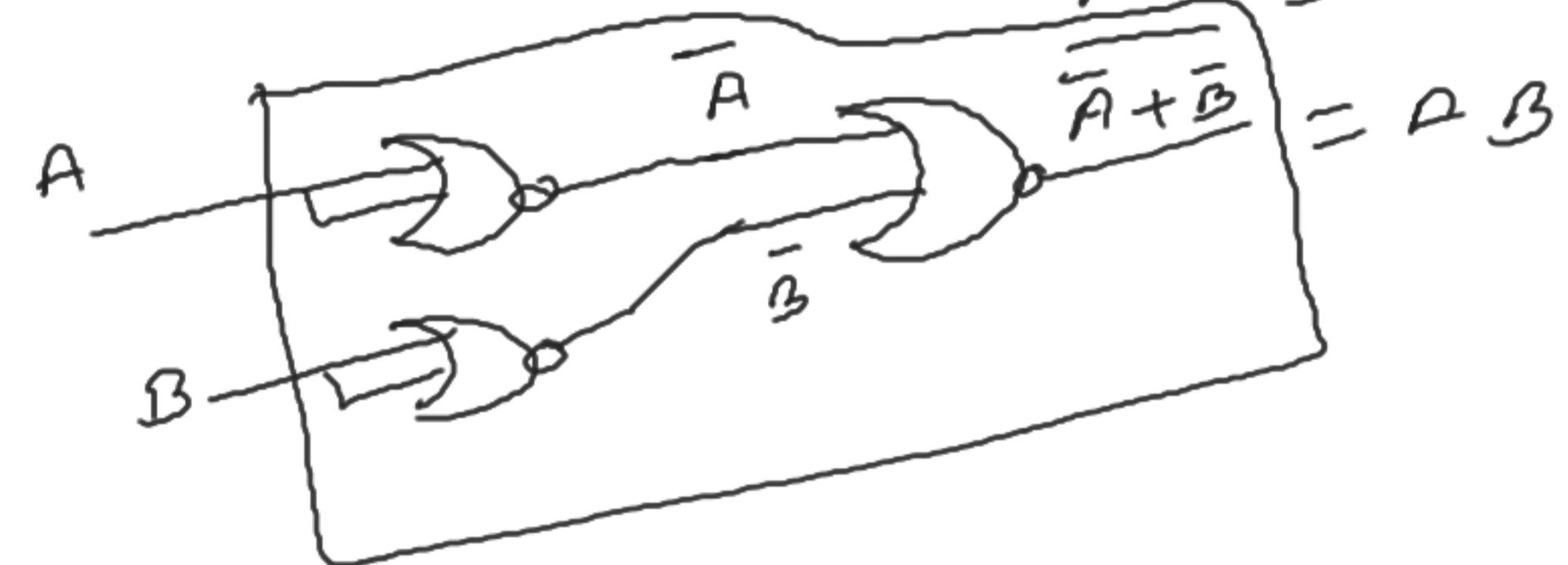3) NOR to AND:



$$\begin{aligned} A &\rightarrow \text{NOR gate} & Y = A \cdot B \\ B &\rightarrow \text{NOR gate} & = \overline{\overline{A} \cdot \overline{B}} \\ && = \overline{\overline{A} + \overline{B}} \end{aligned}$$



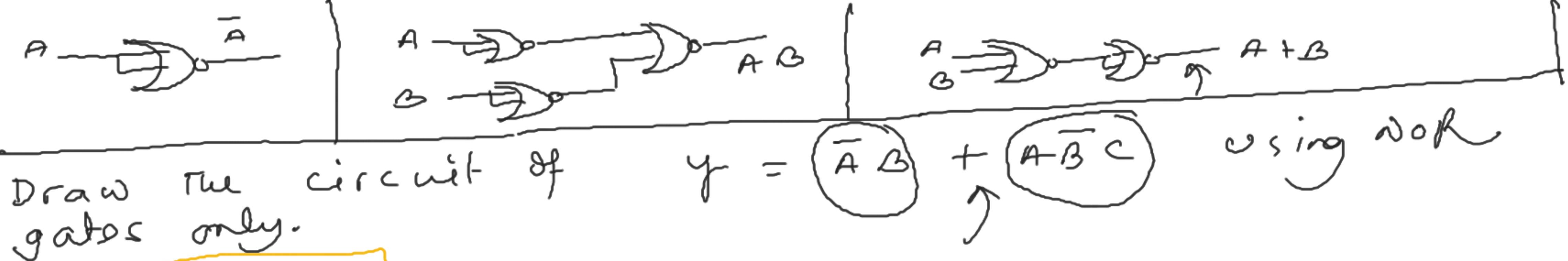We can design all the basic gates using NOR gates only. So NOR gate is the universal gate.




Draw the circuit of
gates only.

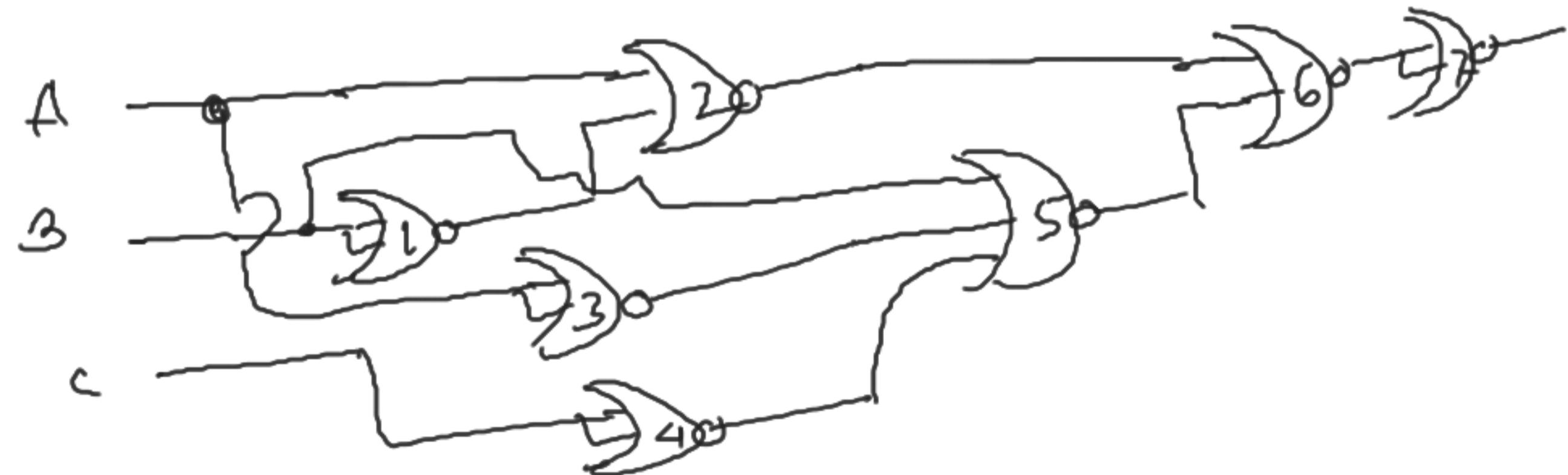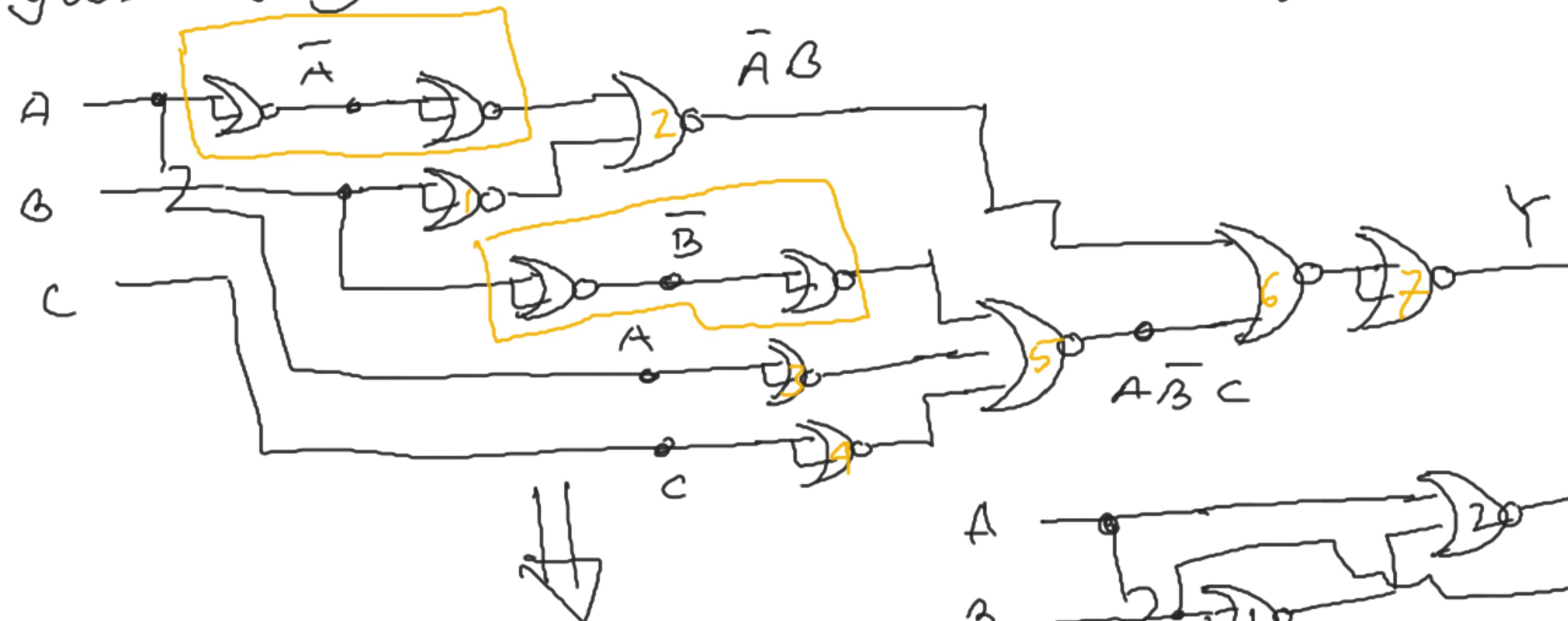

draw the circuit of
NOR gates only.
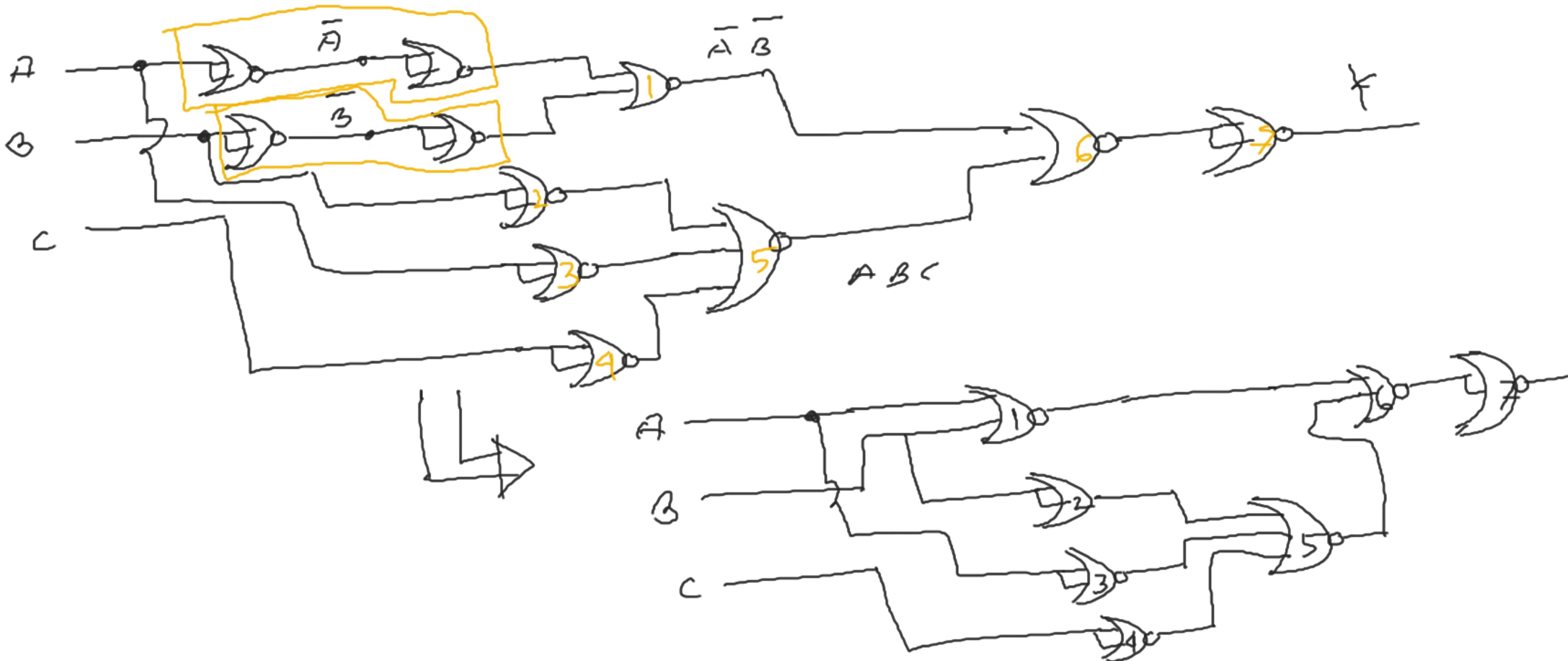
$$Y = \overline{\overline{A}\overline{B}} + \overline{A}\overline{B}C$$



Simplification of logic expression using Karnaugh Map (K-map)

What is K-map?

	$\bar{A}\bar{B}$	$A\bar{B}$	AB	$\bar{A}B$
$\bar{C}D$	1	1	1	1
$C\bar{D}$	1	1	1	1

What is adjacent '1'?

$$\begin{aligned}
 & A\bar{B}\bar{C} + A\bar{B}\bar{C} \\
 & = AB(C + \bar{C}) \\
 & = AB
 \end{aligned}$$

2x4 K-map

	$\bar{A}\bar{B}$	$A\bar{B}$	AB	$\bar{A}B$
$\bar{C}\bar{D}$	1	1	1	x
$\bar{C}D$	1	1	1	1

ABC


$$\begin{aligned}
 & A\bar{B}C\bar{D} + A\bar{B}CD \\
 & = ABC(\bar{D} + D) \\
 & = ABC
 \end{aligned}$$

$$\begin{aligned}
 & \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D \\
 & + A\bar{B}CD + ABC\bar{D}
 \end{aligned}$$

Looping:

1. pair \rightarrow 2 adjacent '1'
2. Quad
3. Octec

9x9 K-map

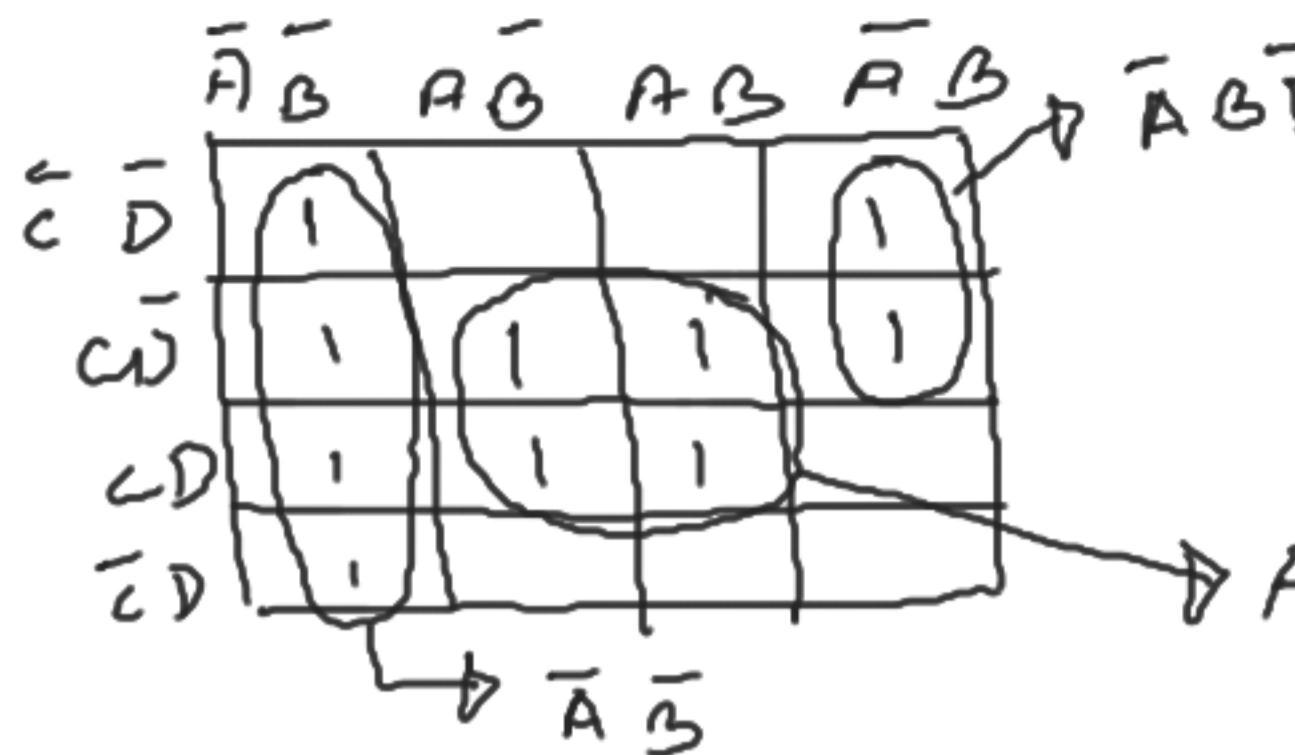

1. Pair \rightarrow 2 adjacent '1's
2. Quad \rightarrow 4 adjacent '1's

$$\begin{aligned}
 & \left. \begin{aligned}
 &= A'\bar{B}\bar{C}\bar{D} + A\bar{B}C\bar{D} + A\bar{B}C\bar{D} + ABCD \\
 &= AC\bar{D}(\bar{B}+B) + ACD(\bar{B}+B) \\
 &= AC\bar{D} + ACD \\
 &= AC(\bar{D}+D) \\
 &= AC
 \end{aligned} \right\}
 \end{aligned}$$

Diagram of a Karnaugh map with variables $\bar{C}\bar{D}$, $C\bar{D}$, CD , $\bar{C}D$ and minterms $\bar{A}\bar{B}\bar{C}\bar{D}$, $\bar{A}\bar{B}C\bar{D}$, $\bar{A}B\bar{C}\bar{D}$, $\bar{A}B\bar{C}D$. Red lines group the first two columns (quad), the last two columns (quad), and the last three columns (pair). The result is $\bar{A}\bar{C}$.

$$\begin{aligned}
 & \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D \\
 &= \bar{A}\bar{C}\bar{D}(\bar{B}+B) + \bar{A}\bar{C}D(B+\bar{B}) \\
 &= \bar{A}\bar{C}\bar{D} + \bar{A}\bar{C}D \\
 &= \bar{A}\bar{C}(\bar{D}+D) \\
 &= \bar{A}\bar{C}
 \end{aligned}$$