
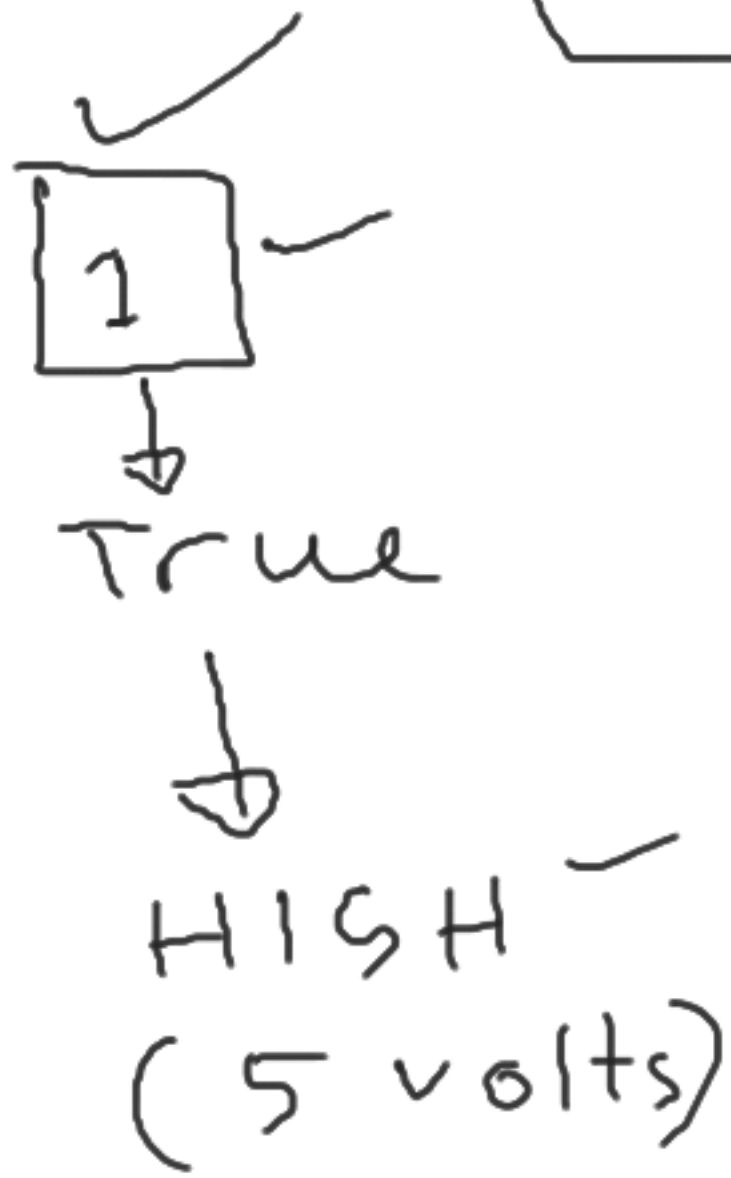



CSE 209 : Digital Logic & System Design (DLSD)

Why DLSD?

Why DLD?

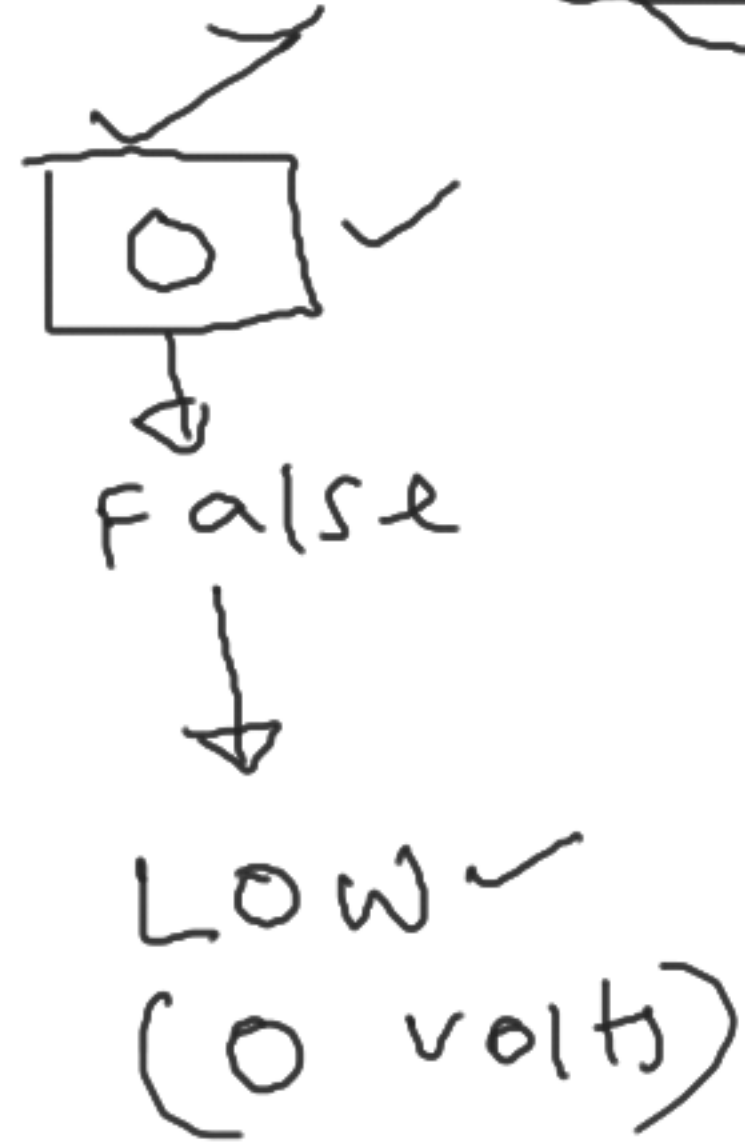

Binary number

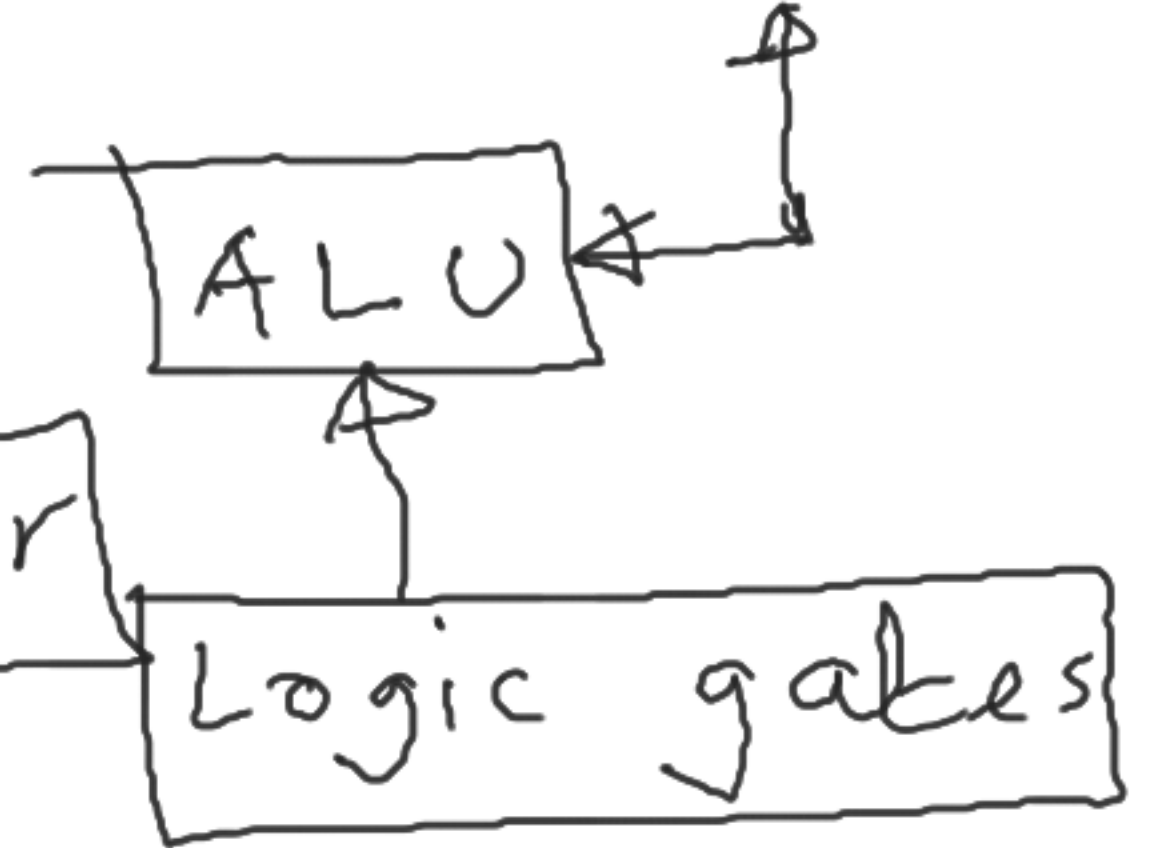

Chapter → 1 and 2

→ Ronal J. Tocci

Chapter 3 : Logic gates & Boolean Algebra


Logic gates :

1. AND gate
(conjunction)

2. OR gate
(Disjunction)

3. NOT gate
(Negation)

1. AND gate :

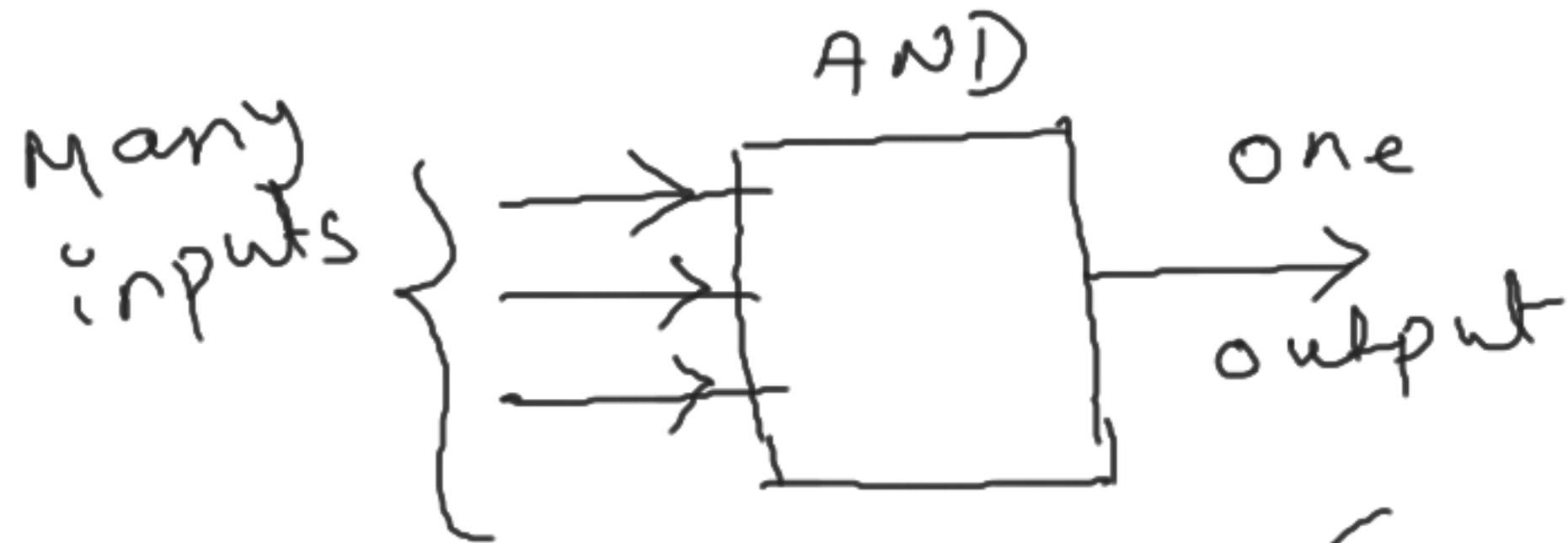

Output will be HIGH when all the inputs are HIGH; otherwise output will be LOW.

Truth Table :

2 inputs

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

• symbol




3 inputs

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Mathematical Notation

$$Y = ABC \quad \bigg| \quad Y = A \cdot B \\ = AB$$

2) OR gate

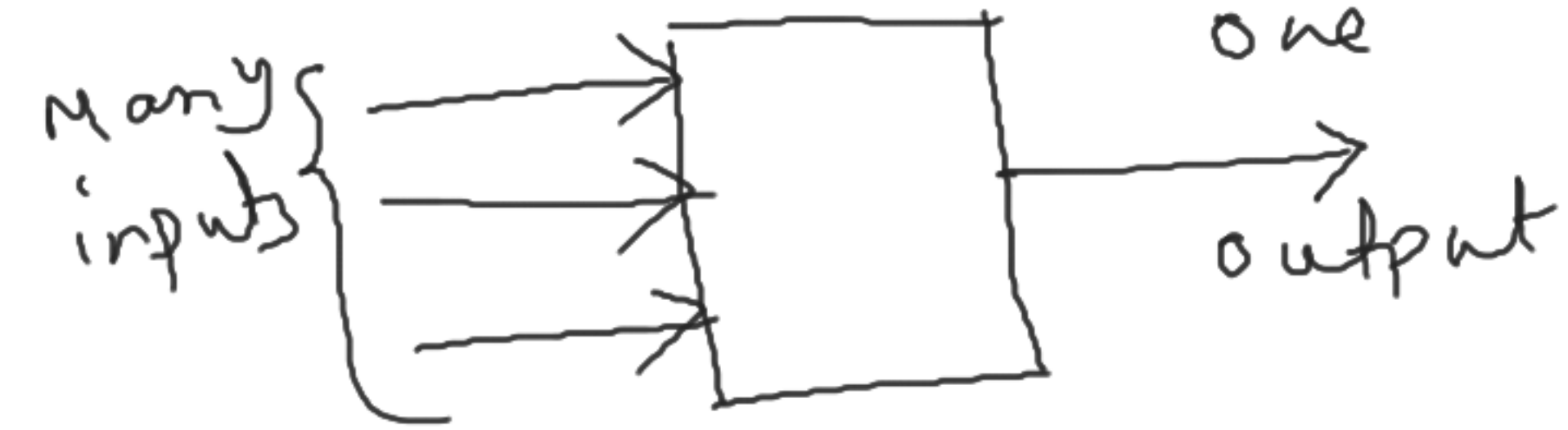

Output will be LOW only when all the inputs are LOW; otherwise output will be HIGH.

Truth Table

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

symbol :




$$Y = A + B$$

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1



$$Y = A + B + C$$

3) NOT gate:


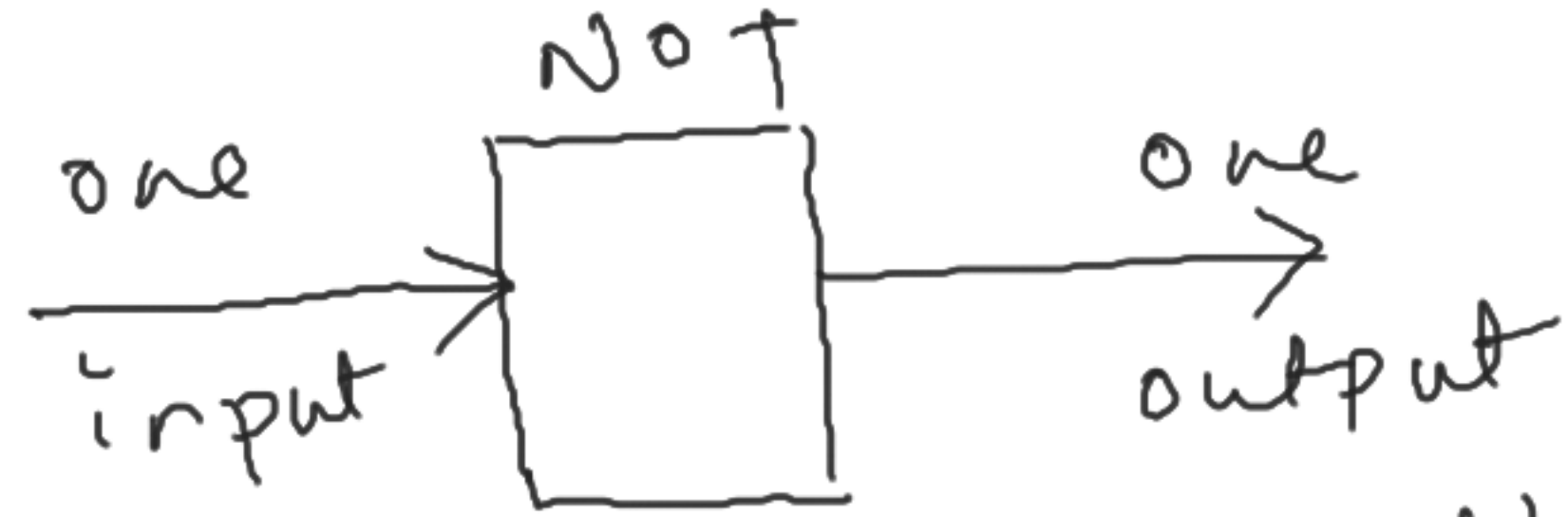


Output will be opposite of input.

Truth Table


A	Y
0	1
1	0

Symbol

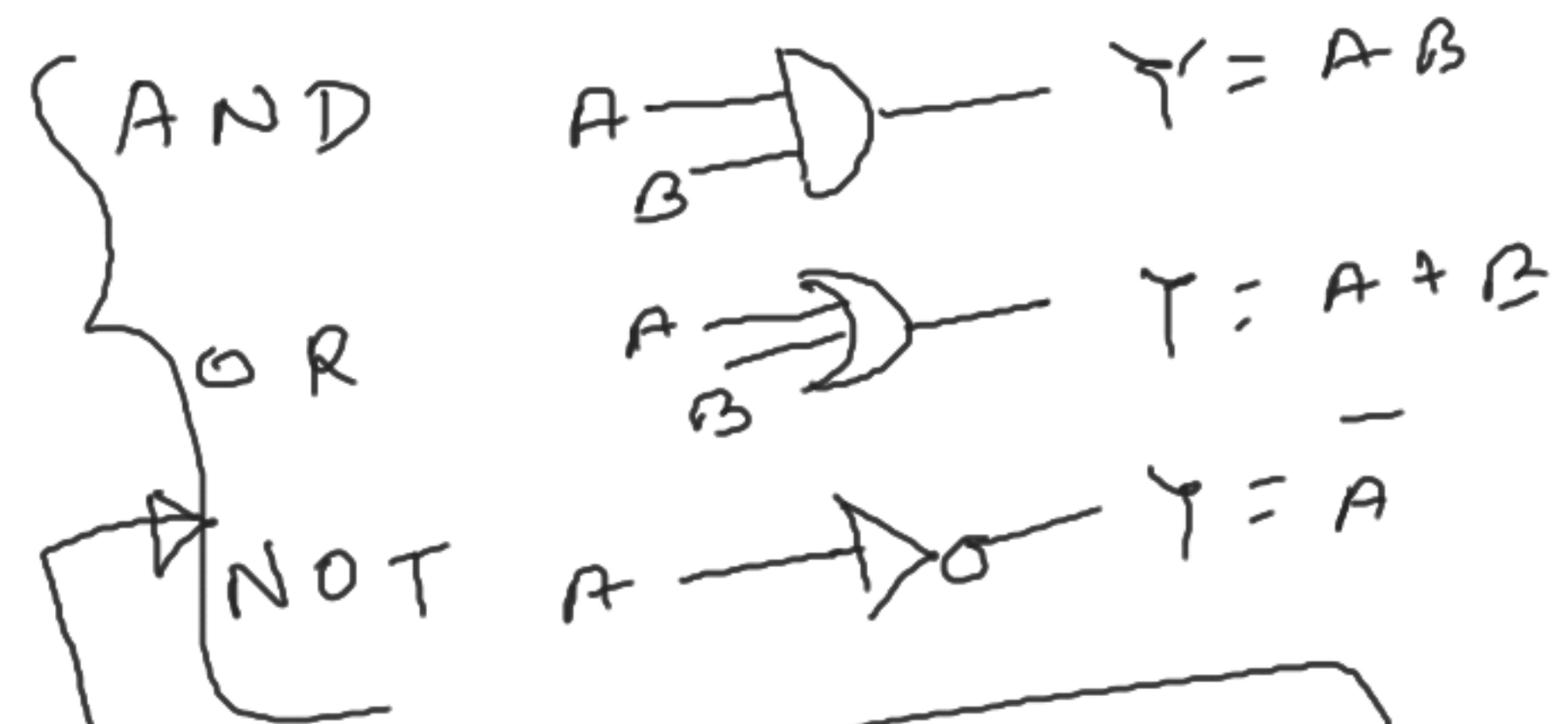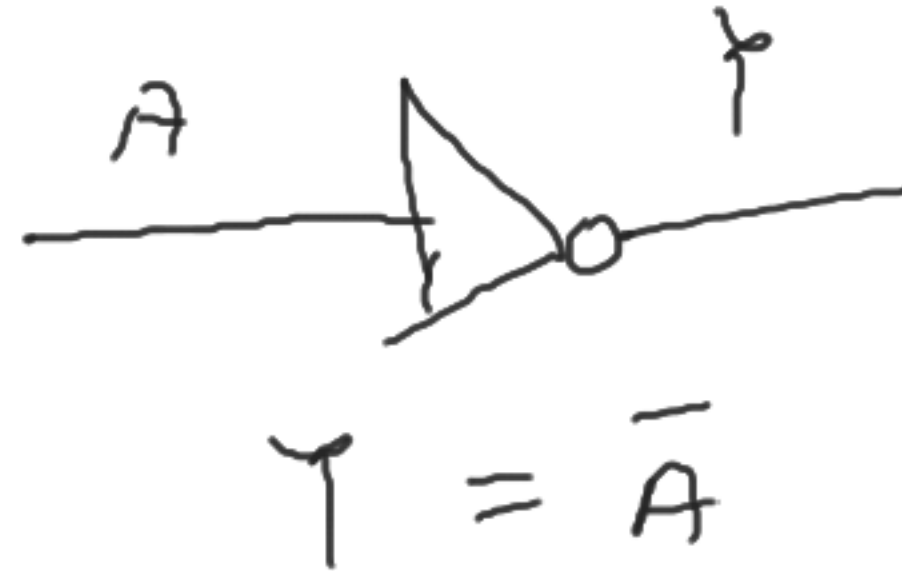

Basic logic gate

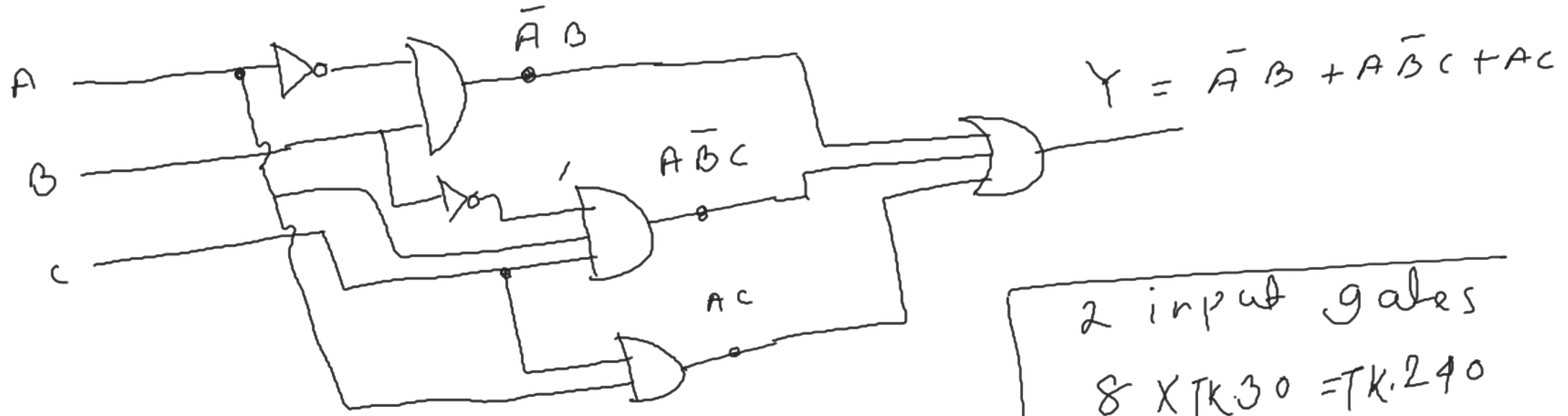Draw the logic circuit of $y = \underline{\bar{A}B} + \underline{A\bar{B}C} + \underline{AC}$




2 input gates
8 X TK.30 = TK.240

Draw The truth Table of $Y = \bar{A}B + A\bar{B}C + AC$

\checkmark A	B	\checkmark C	\checkmark $\bar{A}B$	\checkmark $A\bar{B}C$	\checkmark AC	Y
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	1	0	0	1
0	1	1	1	0	0	1
1	0	0	0	0	0	0
1	0	1	0	1	1	1
1	1	0	0	0	0	0
1	1	1	0	0	1	1

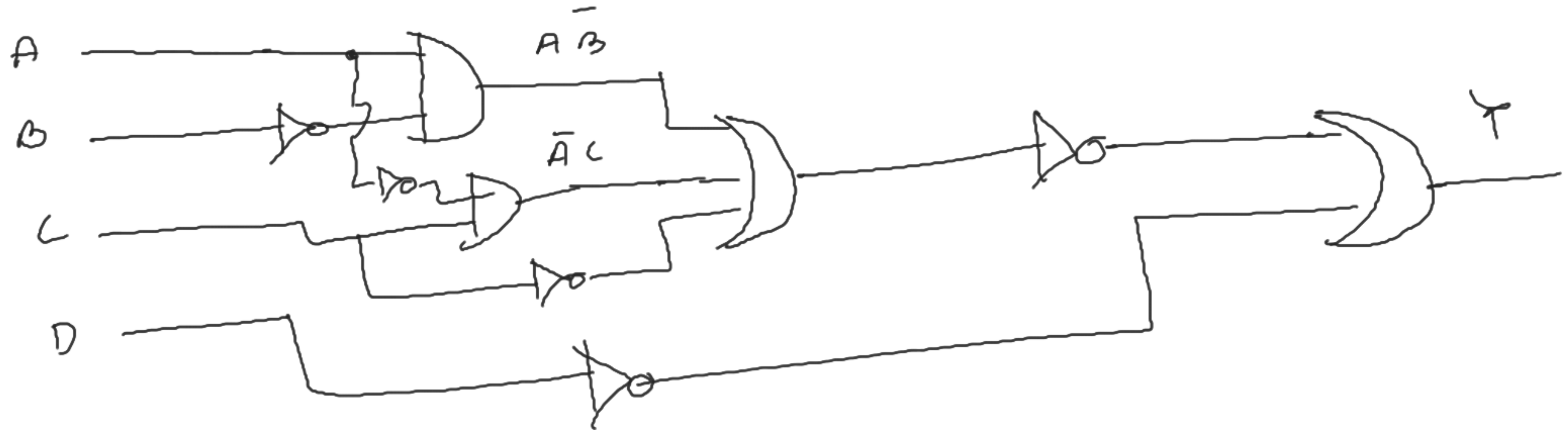$Y = (A\bar{B} + \bar{A}C + \bar{C}) + \bar{D}$
Draw the logic circuit of above expression.




Compound Logic gates:

4. NAND gate 5. NOR gate

6. Exclusive OR gate 7. Exclusive NOR gate.

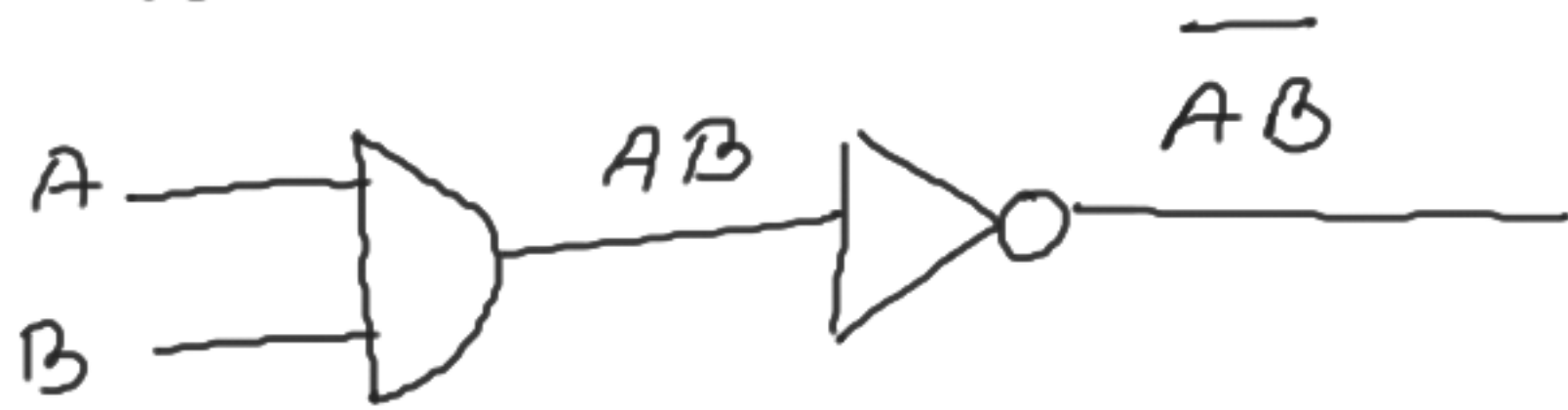4. NAND gate:

$\boxed{\text{NOT}} \text{ AND} = \text{NAND}$




Truth Table:

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

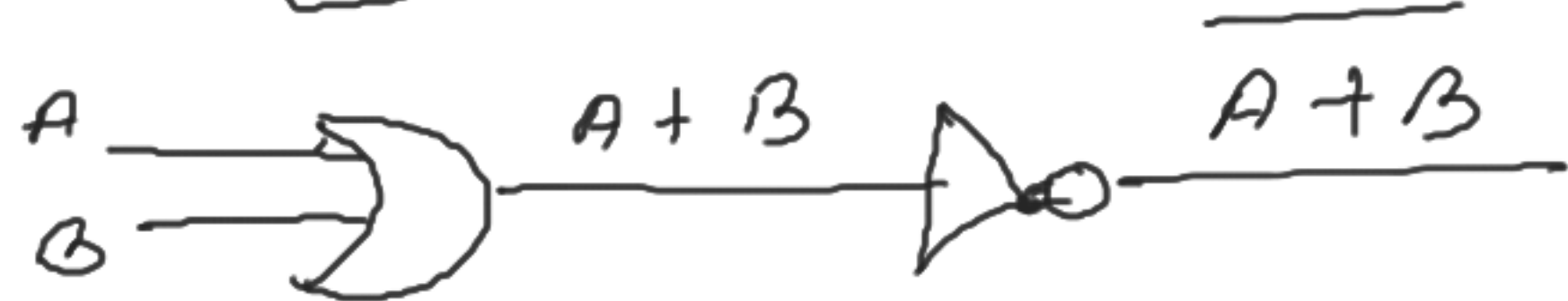5. NOR gate:


$\boxed{\text{NOT}} \text{ OR} \Rightarrow \text{NOR}$



Truth Table:

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

6. Exclusive OR (EX-OR / X-OR) gate:

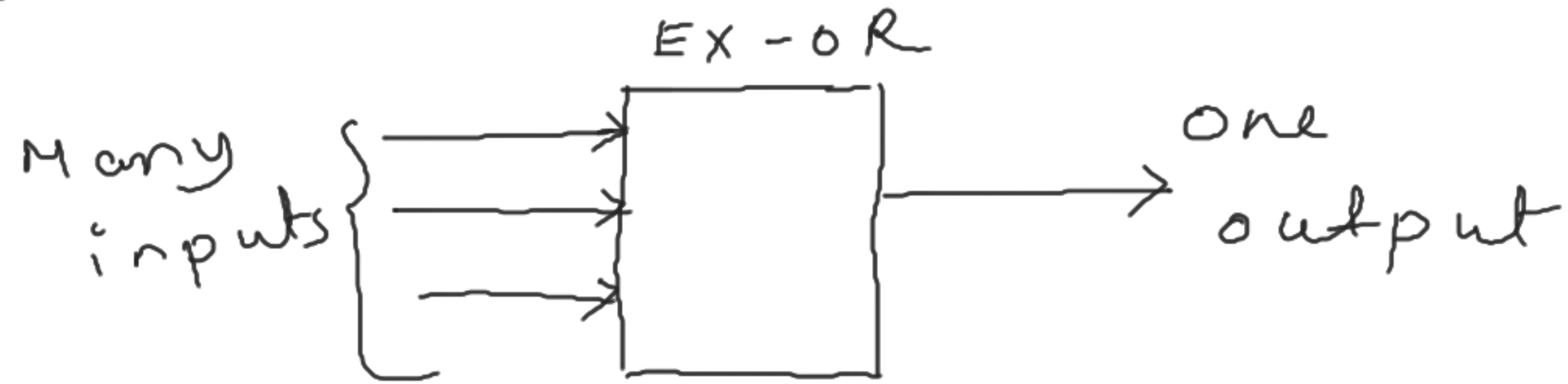

Output will be HIGH when inputs are different, otherwise output will be LOW.

Truth Table:


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

Symbol:



$$Y = A \oplus B$$

7. Exclusive NOR (EX-NOR / X-NOR) gate:

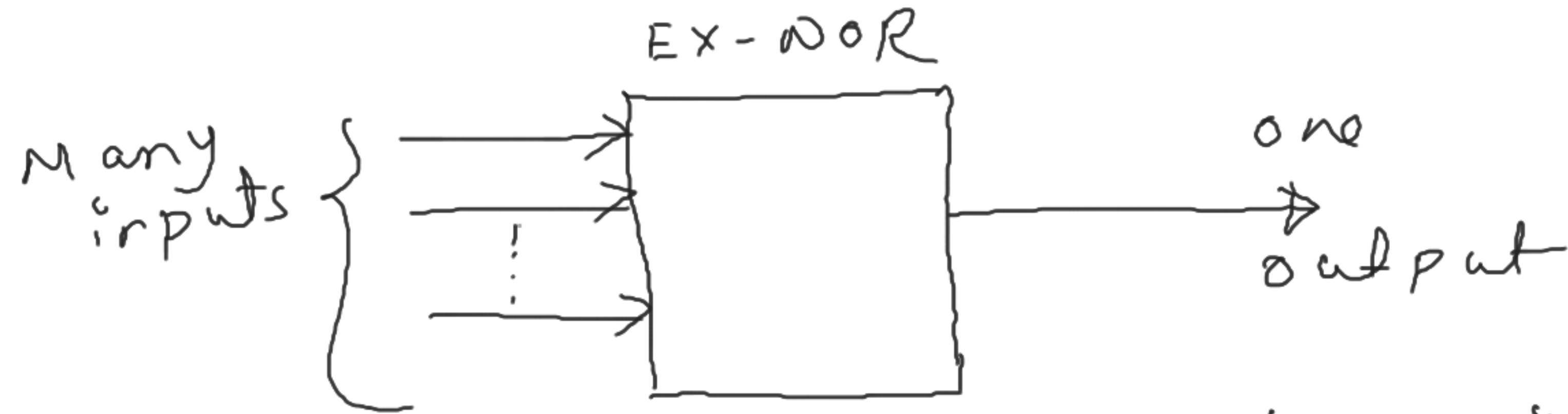

Output will be HIGH when inputs are same, otherwise output will be LOW.

Truth Table

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

symbol:




$$Y = \overline{A \oplus B}$$

Boolean Algebra:


- 1. $x \cdot 0 = 0$
- 2. $x \cdot 1 = x$
- 3. $x \cdot x = x$
- 4. $x \cdot \bar{x} = 0$

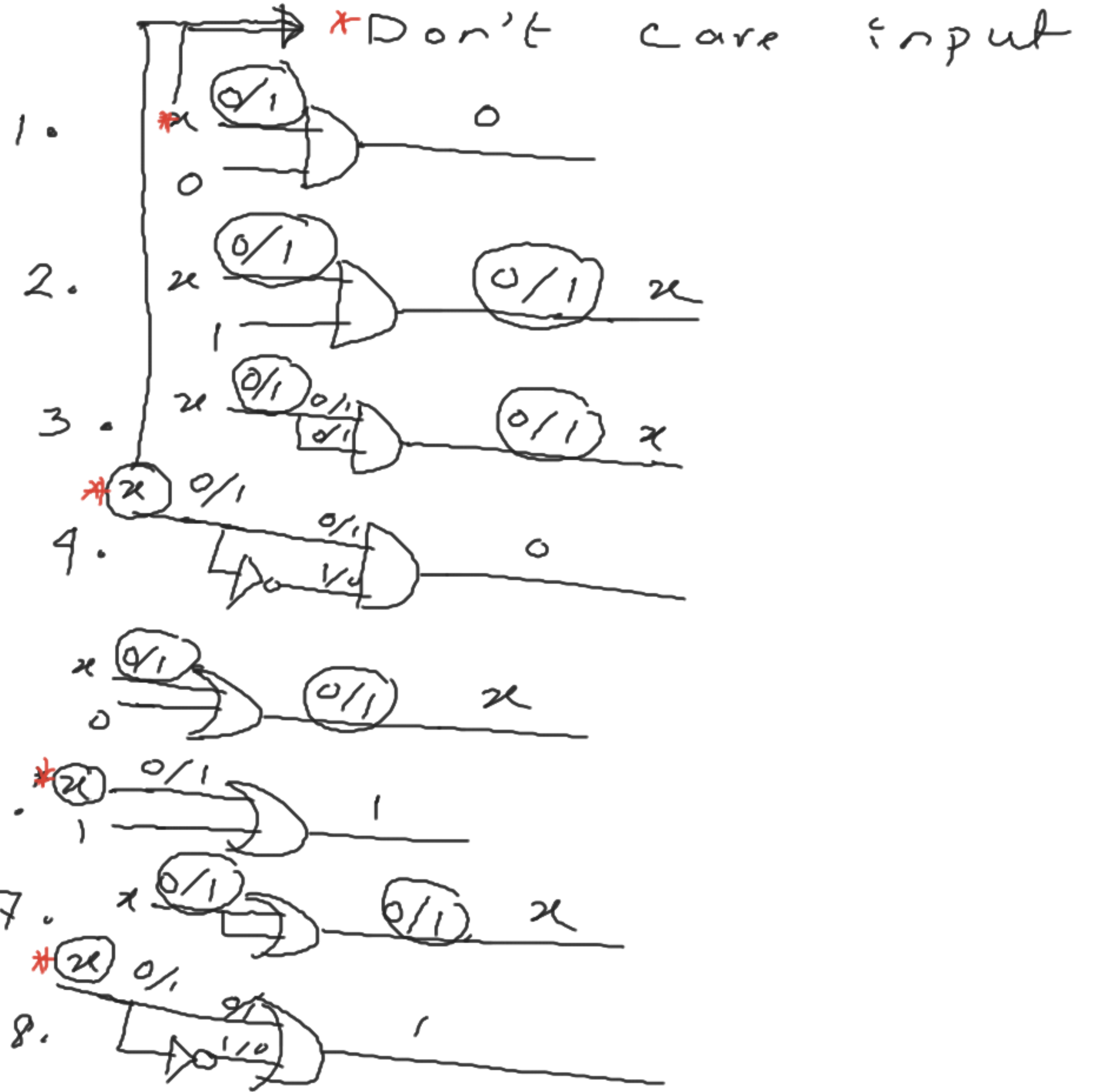- 5. $x + 0 = x$
- 6. $x + 1 = 1$ ✓
- 7. $x + x = x$ ✓
- 8. $x + \bar{x} = 1$ ✓




9) $x + y = y + x$
 10) $x \cdot y = y \cdot x$


Commutative Law

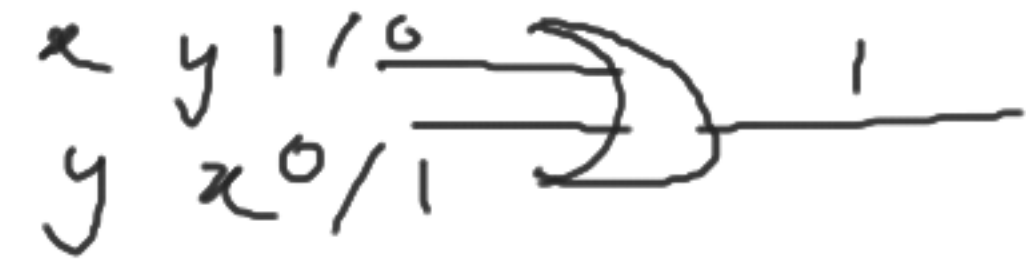

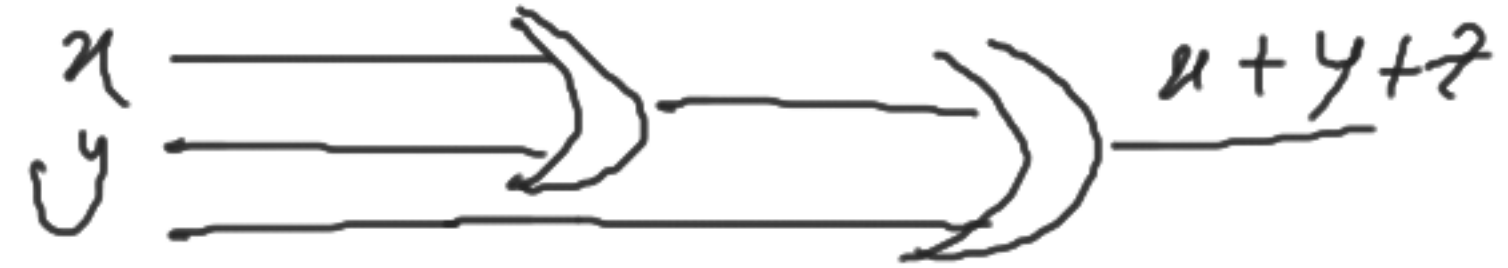11) $x + (y + z) = (x + y) + z = x + y + z$



12) $x(yz) = (xy)z = xyz$

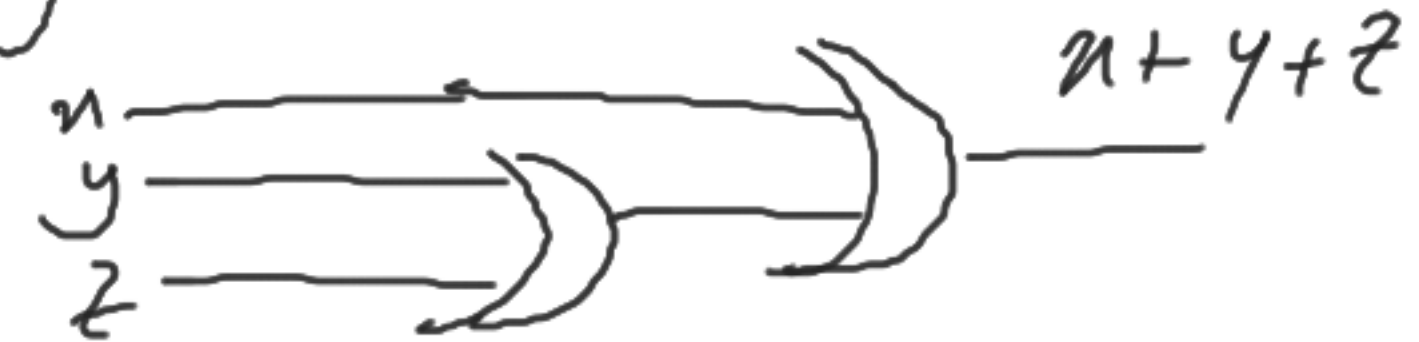

Associative Law

13) a) $x(y + z) = xy + xz$

b) $(x + y)(z + w) = xz + xw + yz + yw$

Distributive Law

14.

$$\underline{x + xy = x}$$

Save 2 logic gates

$$\begin{aligned} & x + xy \\ &= x(1 + y) \\ &= x \cdot 1 \\ &= \underline{\underline{x}} \end{aligned}$$

15) a) $x + \bar{x}y = x + y$
 b) $\bar{x} + xy = \bar{x} + y$ \rightarrow Save 2 logic gates

$$\begin{aligned} & (x) + \bar{x}y \\ &= x + \cancel{xy} + \bar{x}y \\ &= x + y(x + \bar{x}) \\ &= x + y \cdot 1 \end{aligned}$$

$$\begin{cases} x \cdot 1 \\ = x \cdot (1 + y) \\ = x + xy \end{cases}$$

16) $\frac{x+y}{x+y} = \bar{x} \cdot \bar{y}$
 17) $\frac{xy}{xy} = \bar{x} + \bar{y}$ } De Morgan's Theorem

H/w

#simplification of logic expression using Boolean Algebra

$$\begin{aligned} Y &= A \bar{B} D + A \bar{B} \bar{D} \\ &= A \bar{B} (D + \bar{D}) \\ &= A \bar{B} \cdot 1 \\ &= \underline{\underline{A \bar{B}}} \longrightarrow \end{aligned}$$

8 logic gates
8 x TK30 = TK240

2 logic gates
2 x TK.30

= TK. 60

$$\overline{x+y} = \overline{x} \cdot \overline{y}$$

\overline{x}	\overline{y}	$x+y$	$\overline{x+y}$	\overline{x}	\overline{y}	$\overline{x} \cdot \overline{y}$
0	0	0	1	1	1	1
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	0

$$\overline{x+y} = \overline{x} \cdot \overline{y}$$

$$\overline{xy} = \overline{x} + \overline{y}$$

\overline{x}	\overline{y}	xy	\overline{xy}	\overline{x}	\overline{y}	$\overline{x} + \overline{y}$
0	0	0	1	1	1	1
0	1	0	1	1	0	1
1	0	0	1	0	1	1
1	1	1	0	0	0	0

$$\overline{xy} = \overline{x} + \overline{y}$$

$$\begin{aligned}
 Z &= (\bar{A} + B)(A + B) \longrightarrow 4 \text{ logic gates} \\
 &= A\bar{A} + \bar{A}B + AB + BB \longrightarrow \text{Distributive Law} \\
 &= 0 + \bar{A}B + AB + B \\
 &= B(A + \bar{A}) + B \\
 &= B \cdot 1 + B \\
 &= B + B \\
 &= \underline{\underline{B}}
 \end{aligned}$$

$x \cdot x = x$

$$\begin{aligned}
 X &= A\bar{C}D + \bar{A}B\bar{C}D \longrightarrow 7 \text{ logic gates} \\
 &= CD(A + \bar{A}B) \\
 &= \bar{C}D(A + B) \longrightarrow 3 \text{ logic gates} \\
 &= \underline{A\bar{C}D} + \underline{B\bar{C}D} \longrightarrow 5 \text{ logic gates}
 \end{aligned}$$

$$\begin{aligned}
 y &= (\bar{A} + C) \cdot (B + \bar{D}) \\
 &= \bar{A} + C + B + \bar{D} \\
 &= \bar{A} \cdot \bar{C} + \bar{B} \cdot \bar{D} \\
 &= A\bar{C} + \bar{B}D
 \end{aligned}$$

$$\begin{aligned}
 (A) + A(\bar{B}CD) \\
 &= A + BCD
 \end{aligned}$$

$$\begin{aligned}
 (\bar{A}) + A(CDEF) \\
 &= \bar{A} + CDEF
 \end{aligned}$$

$$x + \bar{x}y = x + y$$

$$\bar{x} + x\bar{y} = \bar{x} + y$$

$$1 + \bar{x}y = 1$$

$$\begin{aligned}
 y &= ABC + A\bar{B} \cdot (\bar{A} \cdot \bar{C}) \\
 &= ABC + A\bar{B}(\bar{A} + \bar{C}) \\
 &= ABC + A\bar{B}(A + C) \\
 &= ABC + AA\bar{B} + A\bar{B}C \\
 &= ABC + A\bar{B} + A\bar{B}C \\
 &= ABC + A\bar{B}(1 + C) \\
 &= ABC + A\bar{B}
 \end{aligned}$$

$$= ABC + A\bar{B}$$

$$= A(\bar{B} + BC)$$

$$= A(\bar{B} + C) \checkmark \checkmark$$

$$= A\bar{B} + AC \checkmark$$

$$Z = A\bar{B}\bar{C} + A\bar{B}C + AB\bar{C}$$

$$A(\bar{B} + C)$$

$$= A\bar{B}(\bar{C} + C) + AB\bar{C}$$

$$= A\bar{B} + AB\bar{C}$$

$$= A(\bar{B} + B\bar{C})$$

$$= A(\bar{B} + C) \checkmark$$

$$Y = \bar{A}C(\bar{A}BD) + \bar{A}B\bar{C}\bar{D} + A\bar{B}\bar{C}$$

$$= \bar{A}C(A + \bar{B} + \bar{D}) + \bar{A}B\bar{C}\bar{D} + A\bar{B}\bar{C}$$

$$= A\bar{A}C + \bar{A}\bar{B}C + \bar{A}C\bar{D} + \bar{A}B\bar{C}\bar{D} + A\bar{B}\bar{C}$$

$$= 0 + \bar{A}\bar{B}C + \bar{A}\bar{D}(C + \bar{C}B) + A\bar{B}\bar{C}$$

$$= \bar{A}\bar{B}C + \bar{A}\bar{D}(C + B) + A\bar{B}\bar{C} \checkmark$$

$$= \bar{B}C(\bar{A} + A) + \bar{A}\bar{D}C + \bar{A}\bar{D}B$$

$$= \bar{B}C + \bar{A}C\bar{D} + \bar{A}B\bar{D} = \bar{B}C + \bar{A}\bar{D}(C + B)$$

$$f = \bar{A} B C + A \bar{B} C + \underbrace{A B \bar{C} + A B C}$$

$$= \bar{A} B C + A \bar{B} C + A B (\bar{C} + C)$$

$$= \bar{A} B C + A \bar{B} C + A B$$

$$= \bar{A} B C + A (B + \bar{B} C)$$

$$= \bar{A} B C + A (B + C)$$

$$= \underbrace{\bar{A} B C + A B} + A C$$

$$= B (A + \bar{A} C) + A C$$

$$= B (A + C) + A C$$

$$= A B + B C + A C$$

Design the circuit from the given Truth Table:

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Write down Y as a sum
of product form of A, B, C

$$\begin{aligned} Y &= \bar{A}B\bar{C} + A\bar{B}\bar{C} + AB\bar{C} + ABC \\ &= \bar{A}B\bar{C} + A\bar{B}\bar{C} + AB(\bar{C} + C) \\ &= \bar{A}B\bar{C} + A\bar{B}\bar{C} + AB \\ &= \bar{A}B\bar{C} + A(B + \bar{B}\bar{C}) \\ &= \bar{A}B\bar{C} + A(B + C) \\ &= \bar{A}B\bar{C} + AB + AC \\ &= B(A + \bar{A}C) + AC \\ &= B(A + C) + AC \\ &= AB + BC + AC \end{aligned}$$