

BCD Adder :

what is BCD?

BCD → Binary Coded Decimal
↓
10

Decimal number	Binary code
0 →	0000
1 →	0001
2 →	0010 ✓
3 →	0011
4 →	0100
5 →	0101 ✓
6 →	0110
7 →	0111
8 →	1000
✓9 →	1001
✓0 →	0001 0000

BCD Addition

$$\begin{array}{r}
 43 \\
 + 25 \\
 \hline
 68
 \end{array}
 \quad
 \begin{array}{r}
 0100 \quad 0011 \\
 0010 \quad 0101 \\
 \hline
 0110 \quad 1000
 \end{array}$$


$$\begin{array}{r}
 78 \\
 53 \\
 \hline
 ???
 \end{array}
 \quad
 \begin{array}{r}
 0111 \quad 1000 \\
 0101 \quad 0011 \\
 \hline
 1100 \quad 1011 \\
 0110 \quad 0110 \\
 \hline
 1314
 \end{array}$$

Error?

[If sum > 9]

Error Correction

{ If sum > 9
Then add 6

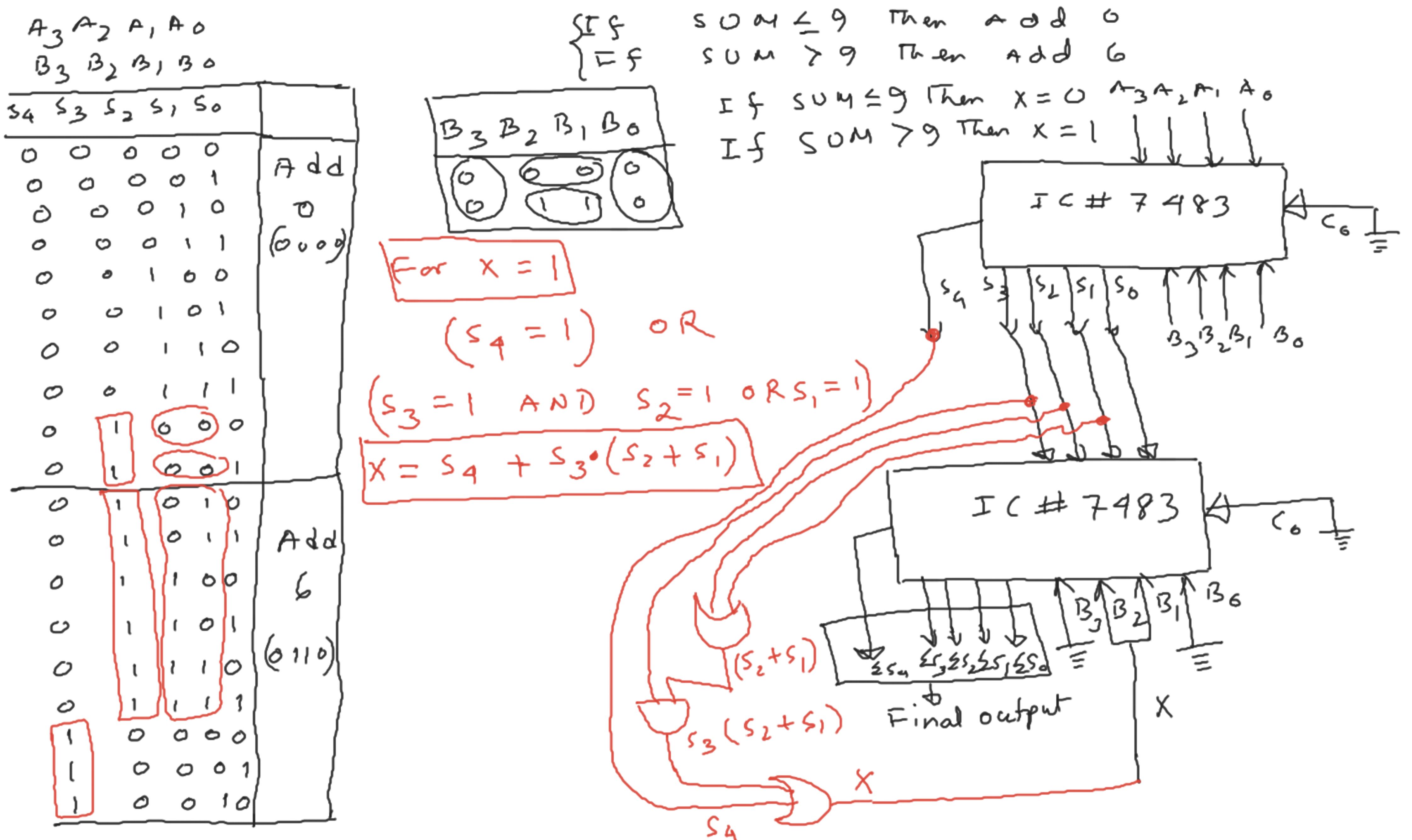


Chapter 5 : Flip Flop and Related Devices

what is Flip Flop?

Assignment 1 : write a short note on flip flop.

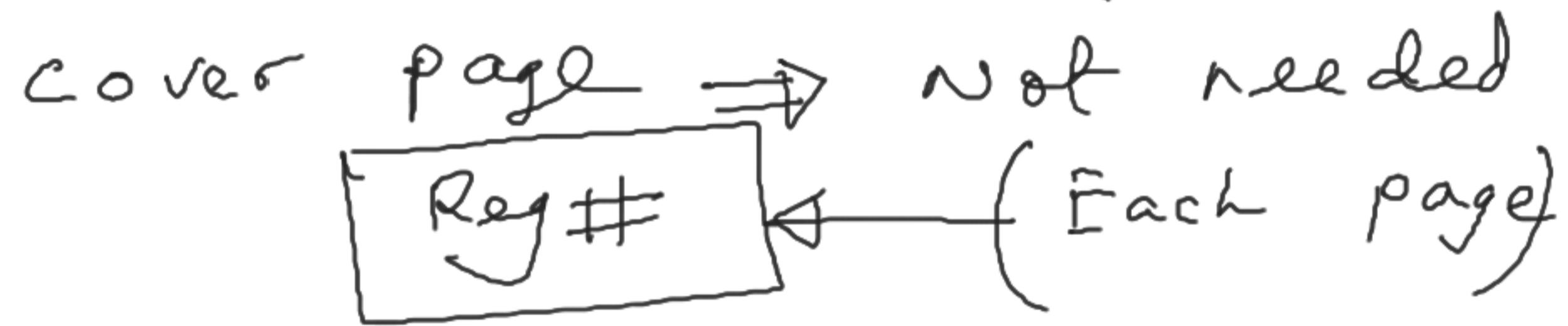
Google \Rightarrow 3 to 4 pages ; 12 font size
single space



Date of submission \Rightarrow 04.02.2021

11 AM


what is Flip Flop?

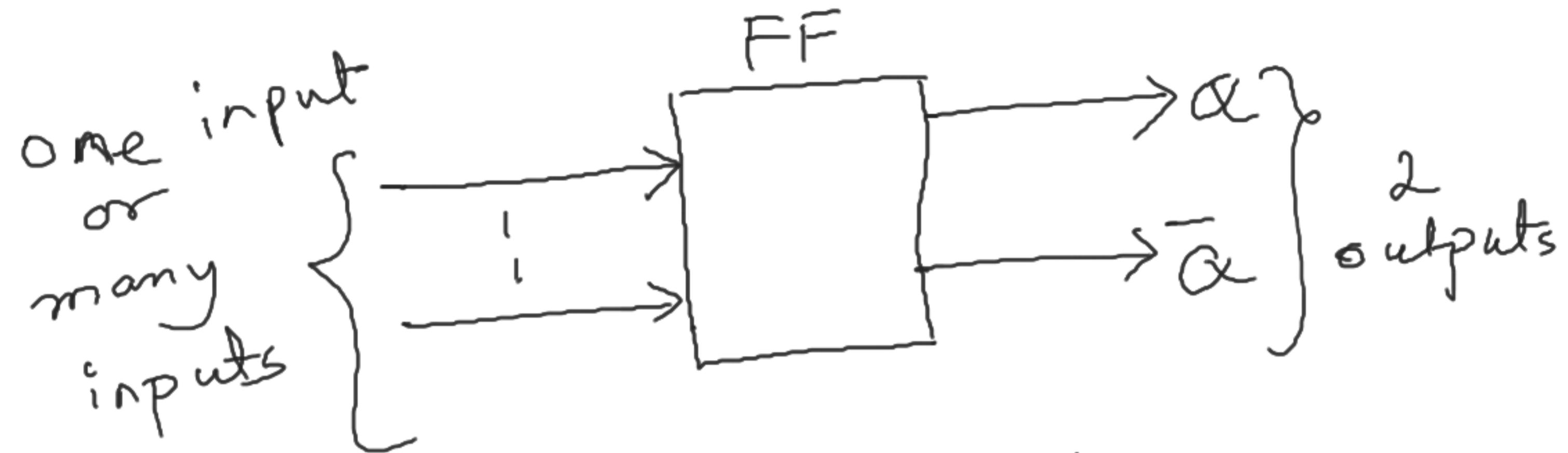

Flip Flop is a device where there is one input or are many input, but exactly have two outputs. One output is opposite of other output.

NAND Latch:

Internal circuit

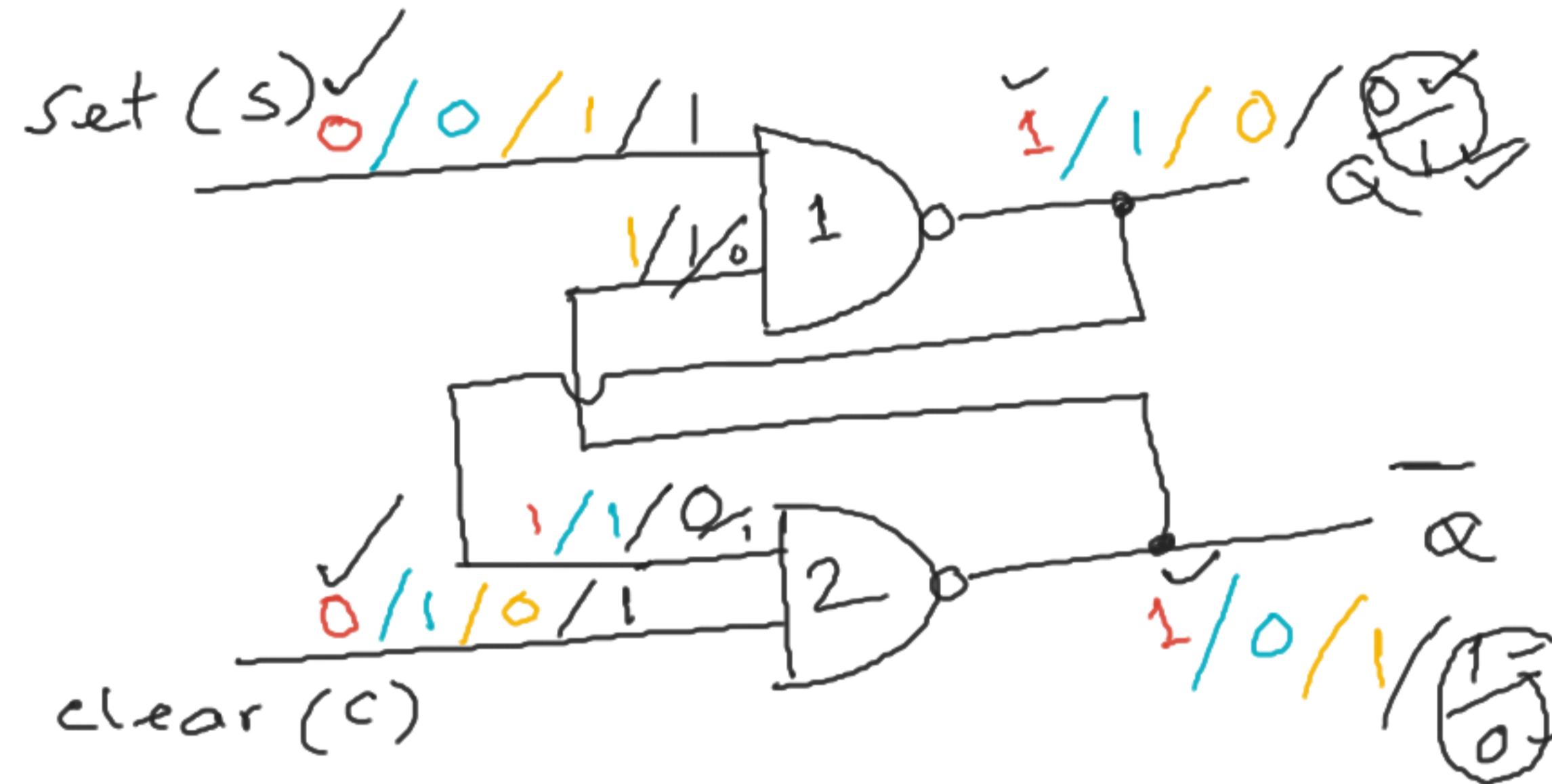

(1, 1) \Rightarrow

If initially $Q = 0$ then finally $Q = 0$
 If $Q = 1$ then $Q = 1$

No change

Truth Table

S	C	Q
0	0	Invalid
0	1	1
1	0	0
1	1	No change

NAND gate


A	B	T
0	0	1
0	1	0
1	0	0
1	1	0

Block diagram




Wave

Truth Table

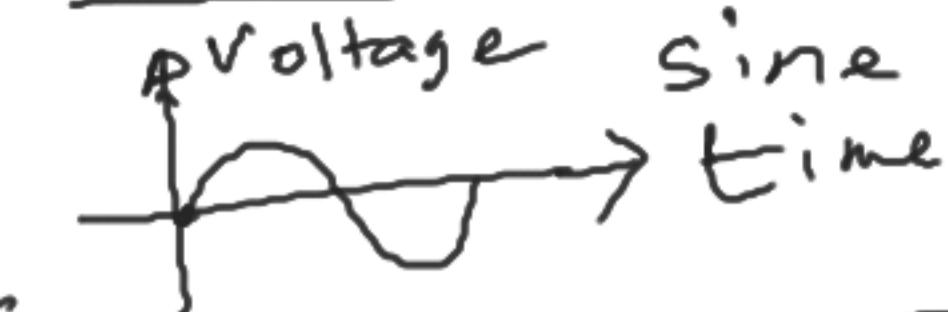

S	C	Q
0	0	Invalid
0	1	-
1	0	0
1	1	No change

Waveform diagram:

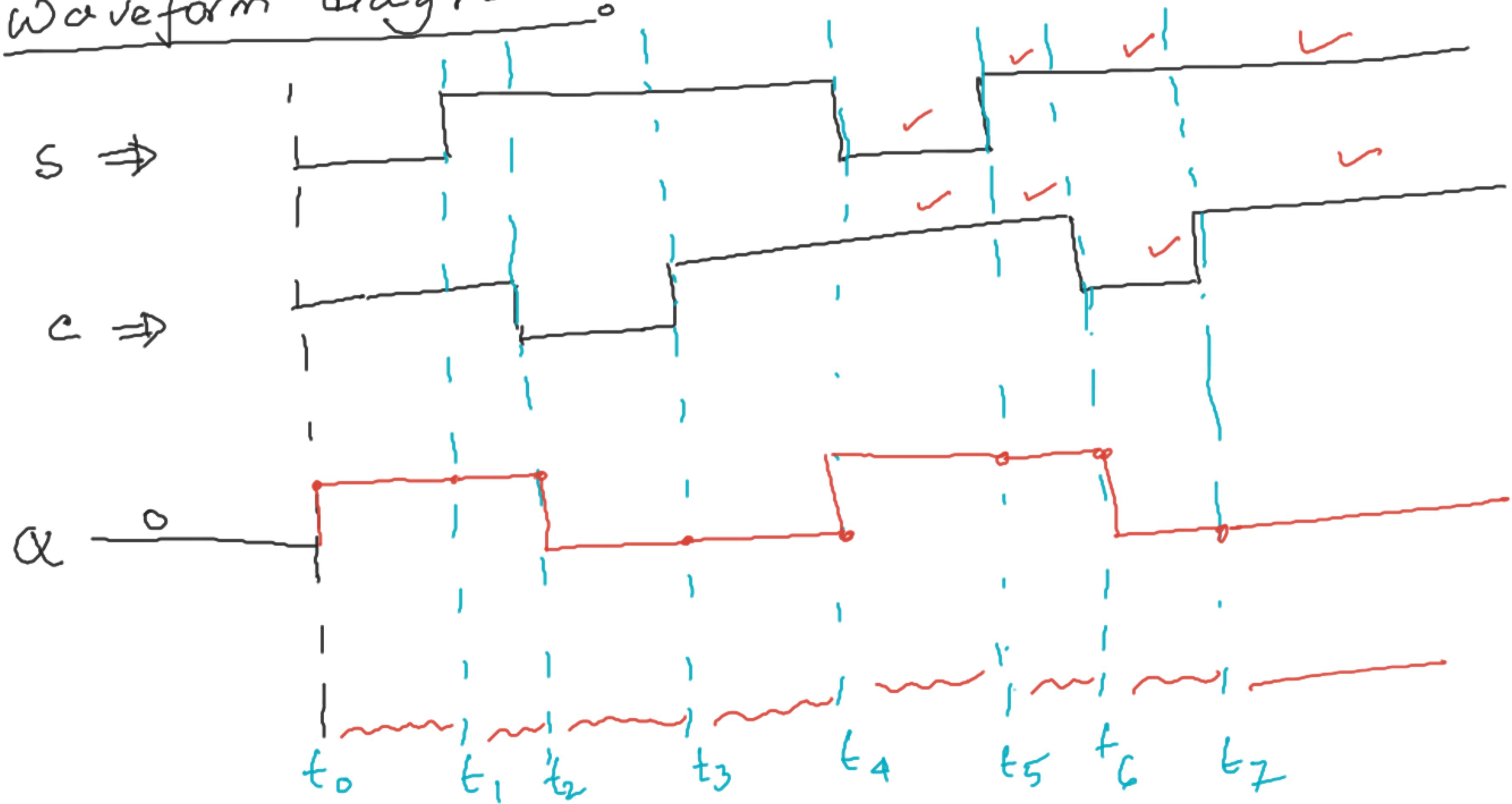


Initially

$$Q = 0$$

Draw The
wave form
of Q

NOR Latch

Internal circuit

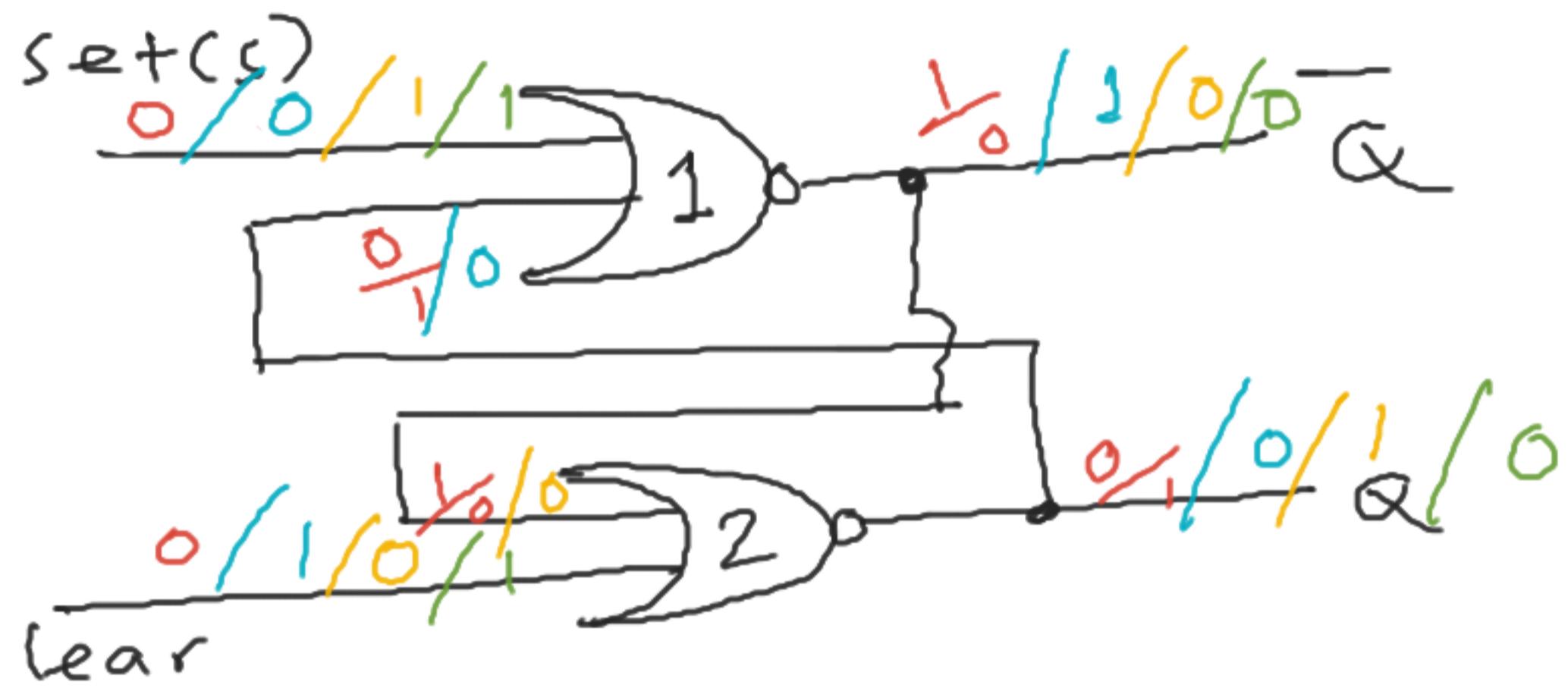

Truth Table

S	C	Q
0	0	No change
0	1	0
1	0	1
1	1	Invalid

$(0, 0)$

If initially $Q = 0$, Then finally $Q = 0$

"

$Q = 1$, "

" $Q = 1$

No

change

NOR gate

A	B	Y
0	0	1




Block diagram



Truth Table



S	C	Q
0	0	No change
0	1	0
1	0	1
1	1	Invalid

Waveform diagram:

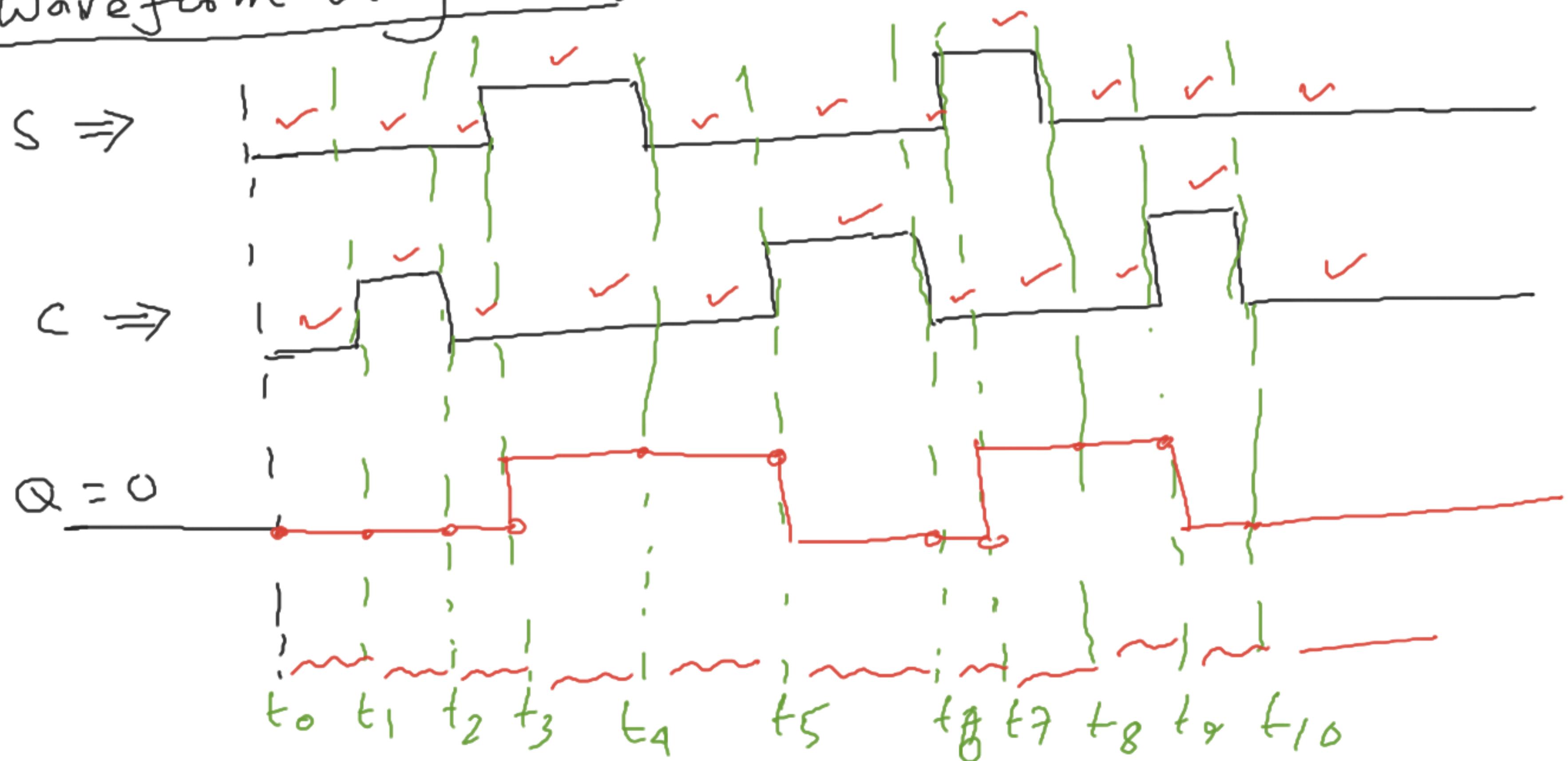

Initially
 $Q = 0$.

Draw The
 wave form
 of Q

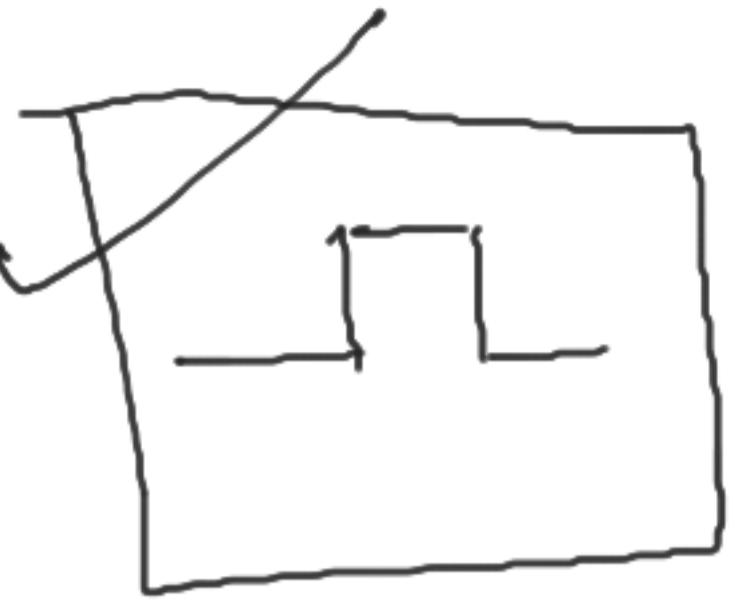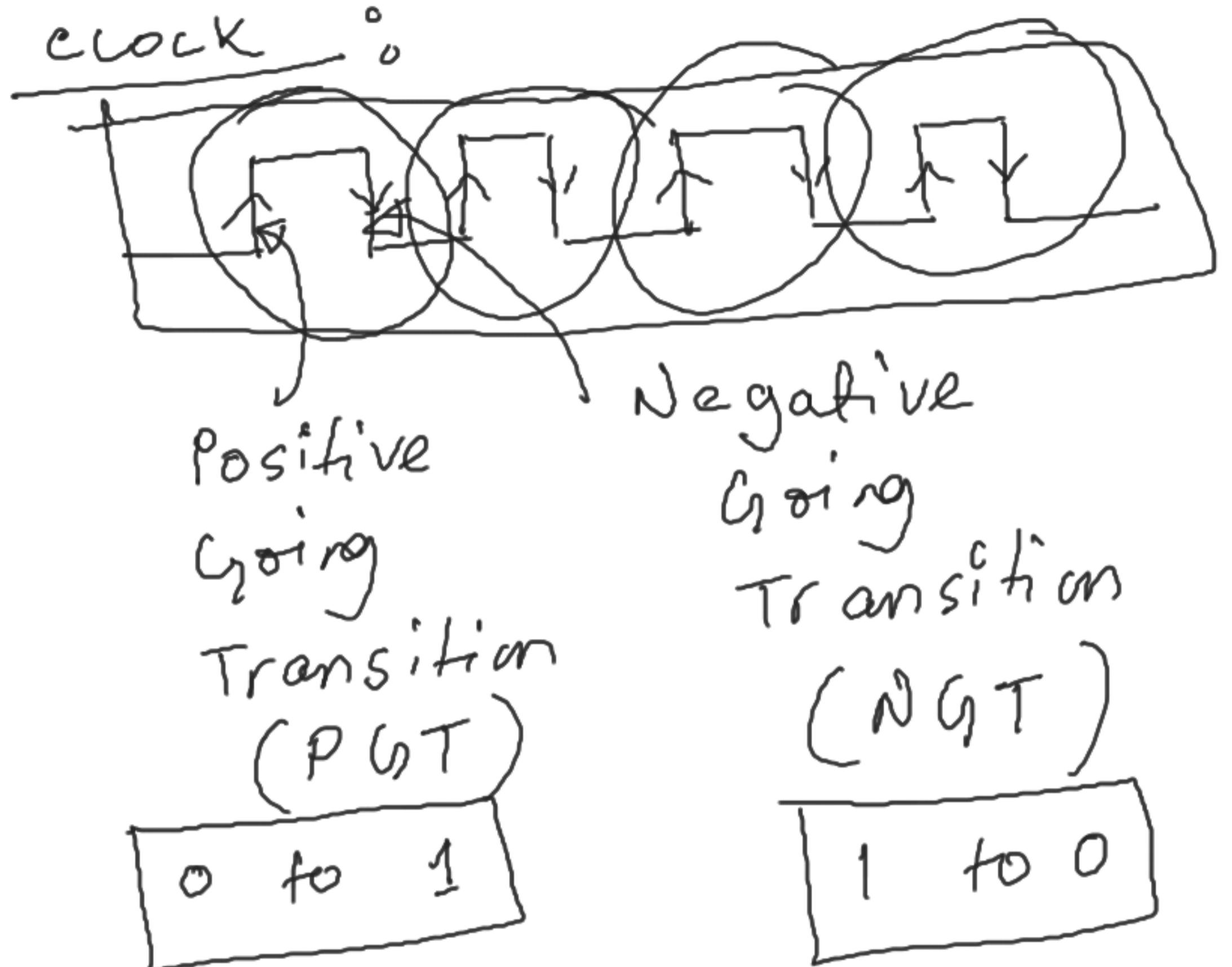

PGT



NGT

Frequency

Number of oscillations cycles per second.

1 Hz → 1 cycle/sec

10 Hz → 10 cycles/sec


1 KHz → 1000 " /sec

1 MHz → 10^6 "


1 GHz → 10^9 "

Clocked SC Flip Flop

Internal circuit

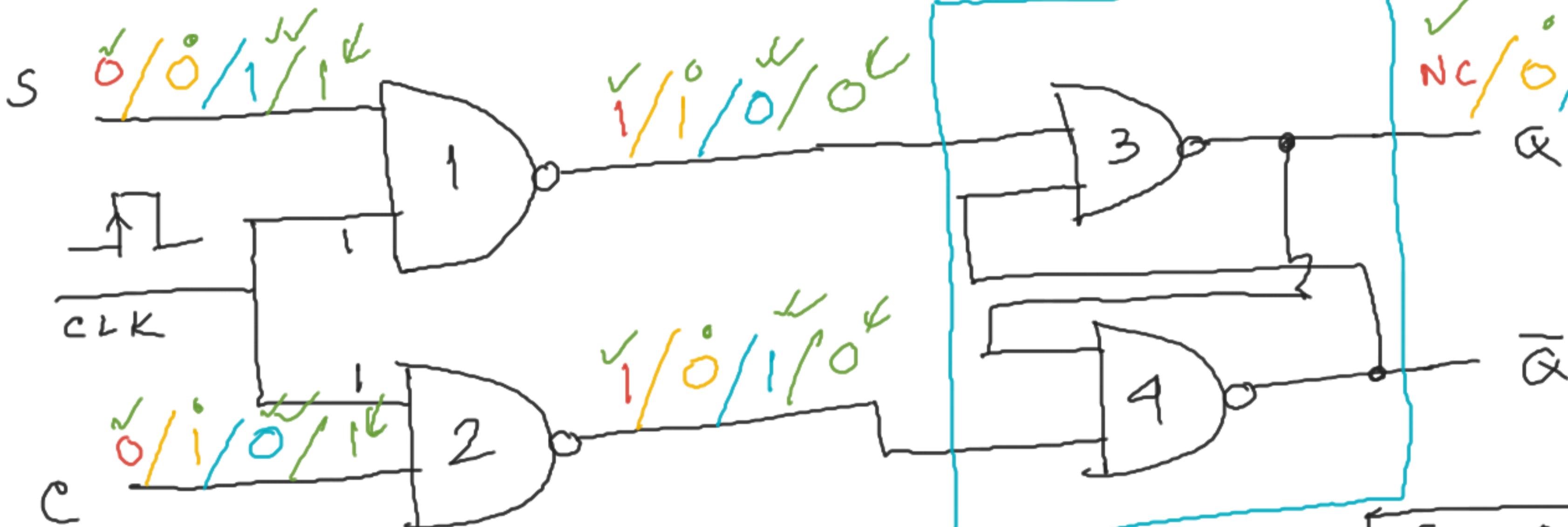

operation :

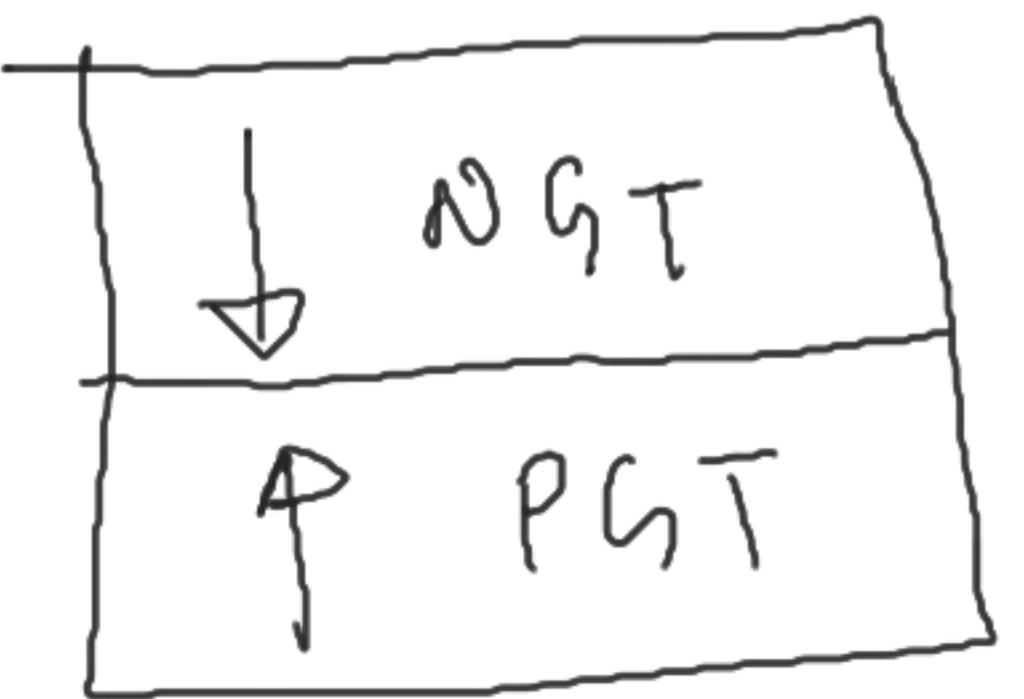


NAND Latch

S	C	Q
✓ 0	0	Invalid
✓ 0	1	1
1	0	0
1	1	N.C.

Truth Table :

S	C	CLK	Q
✓ 0	0	↑	NO change
✓ 0	1	↑	0
1	0	↑	1
✓ 1	1	↑	Invalid


Block Diagram:

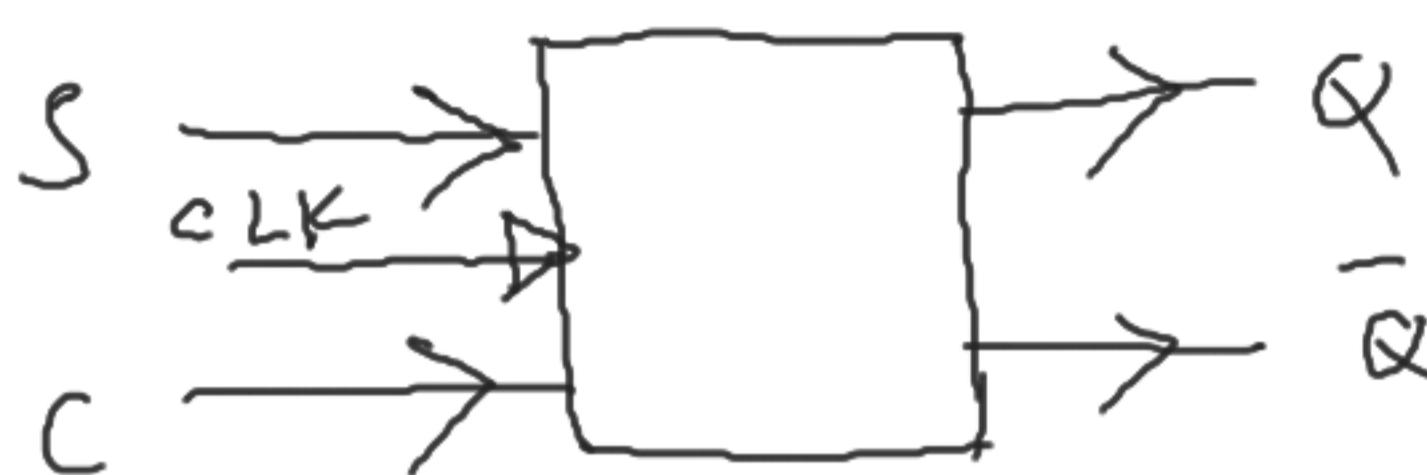


Truth Table

S	C	CLK	Q
0	0	↑	No change
0	1	↑	0
1	0	↑	1
1	1	↑	Invalid

Waveform diagram:

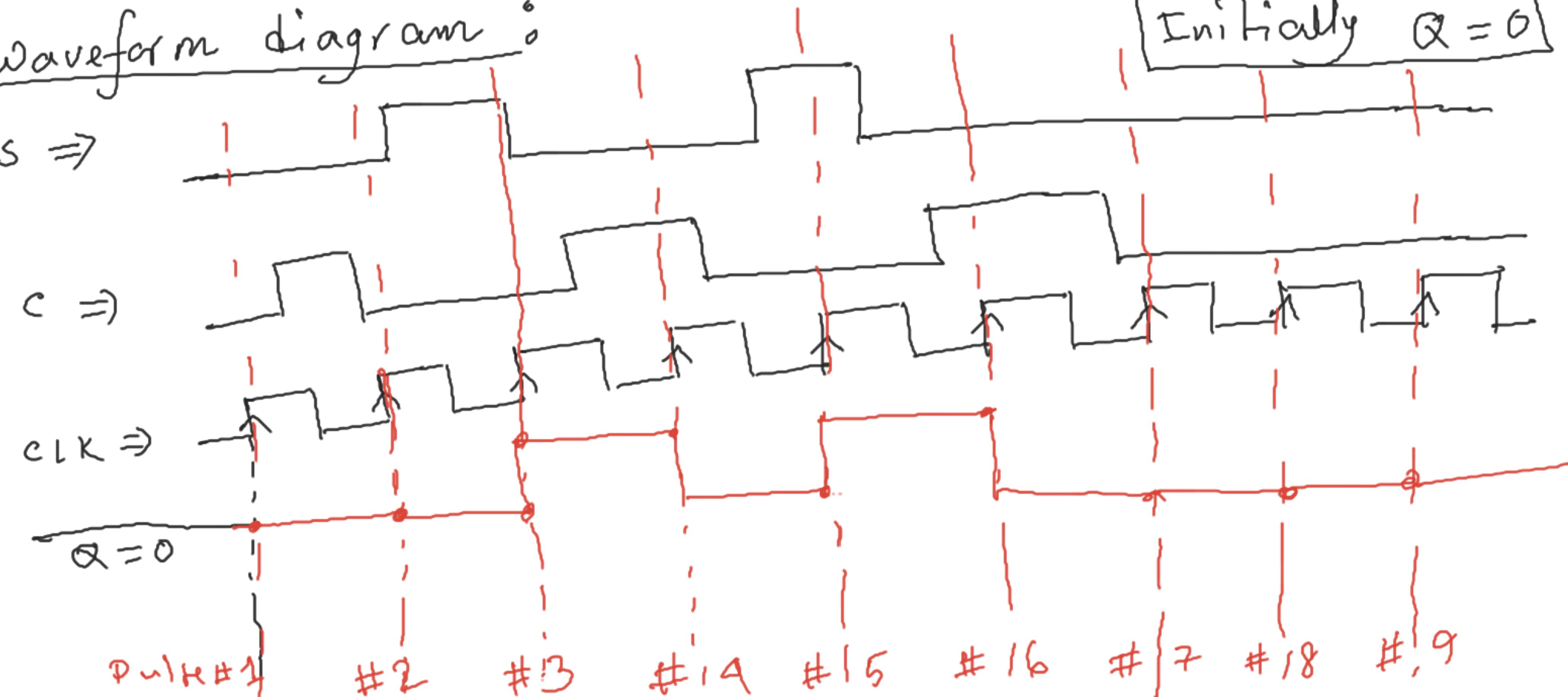


Block diagram:

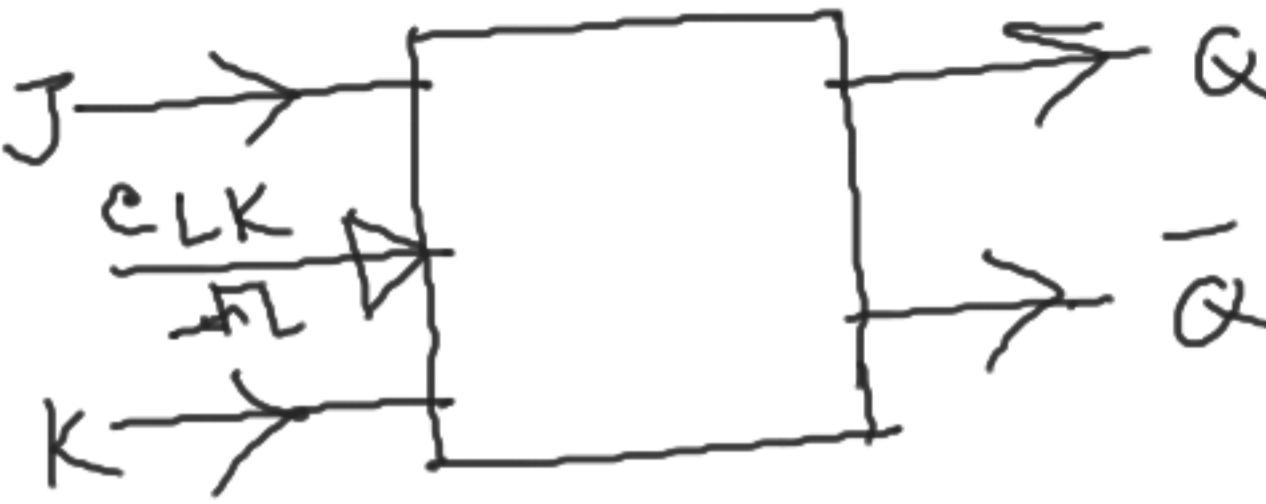

Truth Table


J	K	CLK	Q
0	0	↑	N.C.
0	1	↑	0
1	0	↑	1
1	1	↑	Toggle

Waveform diagram

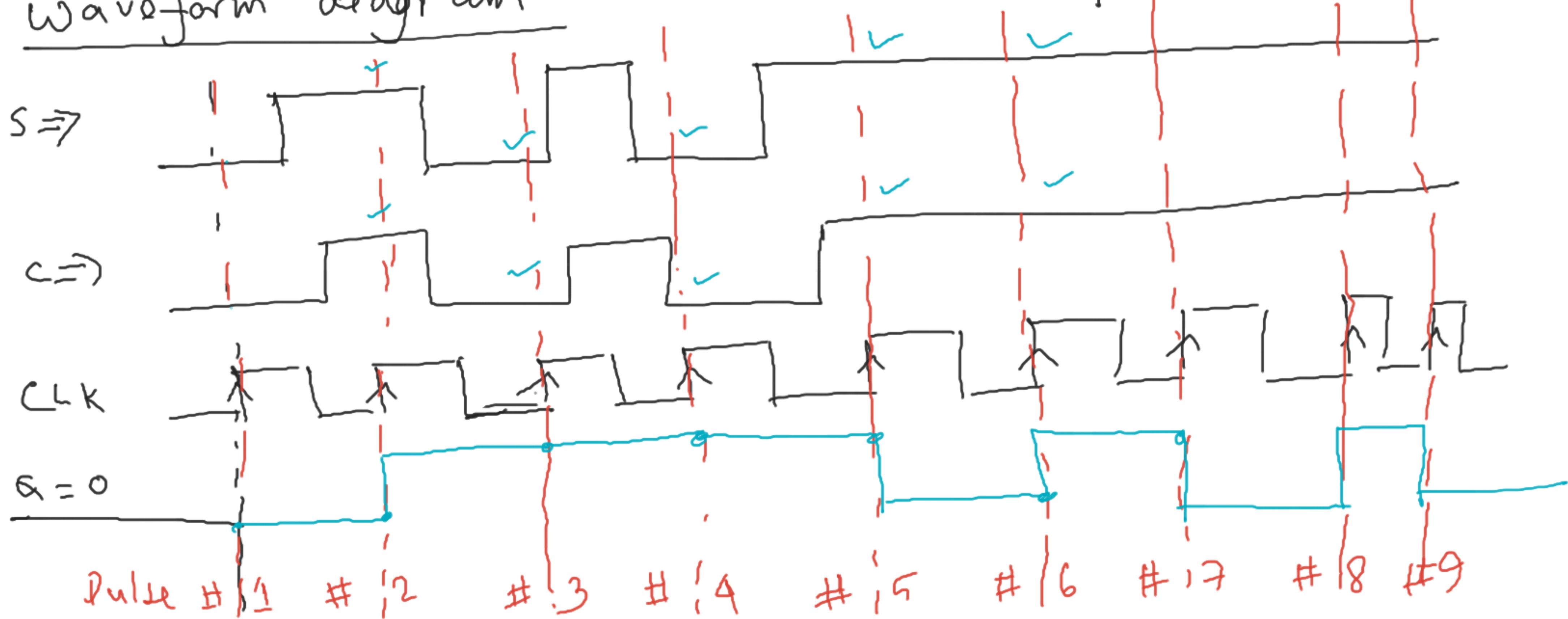

Clocked JK Flip Flop:

Internal circuit

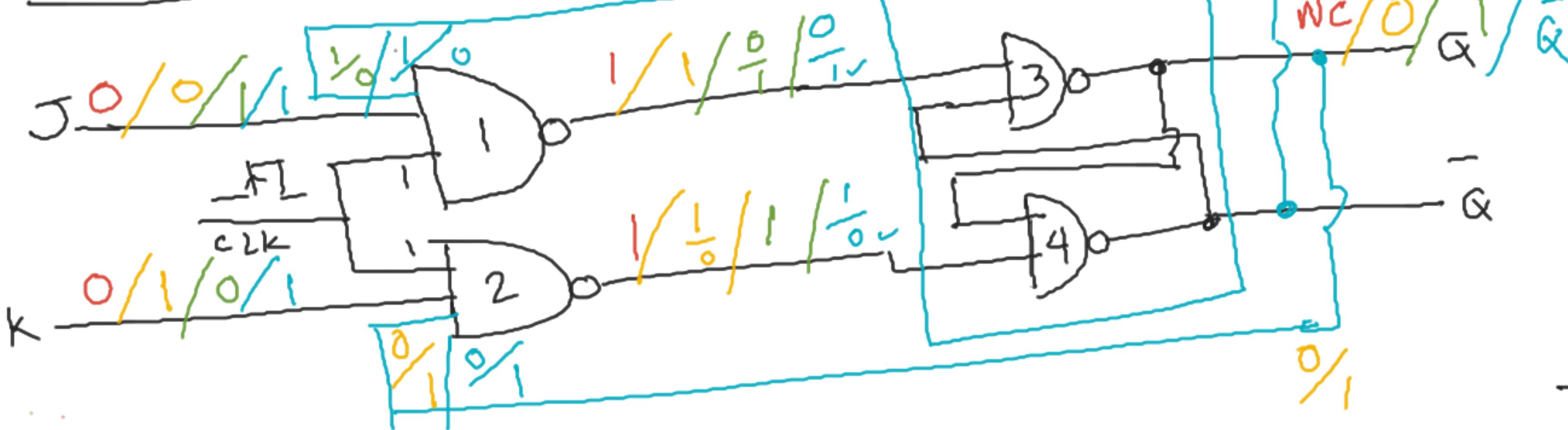

NAND Latch

S	C	Q
0	0	Invalid
0	1	1
1	0	0
1	1	No change

Operation:

$(0, 1) \Rightarrow$ If initially $Q = 0$; finally $Q = 0$ } $Q = 0$

$(1, 0) \Rightarrow$ " " " " $Q = 0$; " " $Q = 1$ } $Q = 1$


$(1, 1) \Rightarrow$ " " " " $Q = 0$; " " $Q = 1$ } \bar{Q}
" " " " $Q = 1$; " " $Q = 0$ } $Q = 0$

Truth Table

J	K	clock	Q
✓ 0	0	↑	No change
✓ 0	1	↑	0
✓ 1	0	↑	1
1 1	1	↑	Toggle

Clocked D Flip Flop :

Internal Circuit

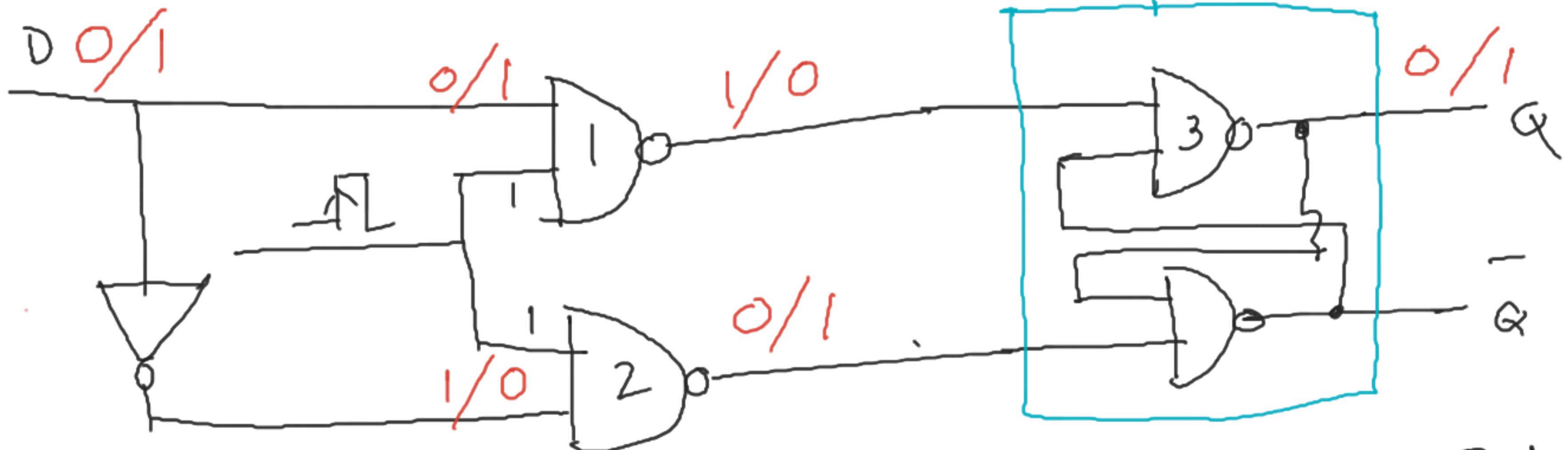


NAND Latch

S	C	Q
0	0	Invalid
0	1	1
1	0	0
1	1	N.C.

Operation and Truth Table :

D	CLK	Q
0	↑	0
1	↑	1



Block Diagram

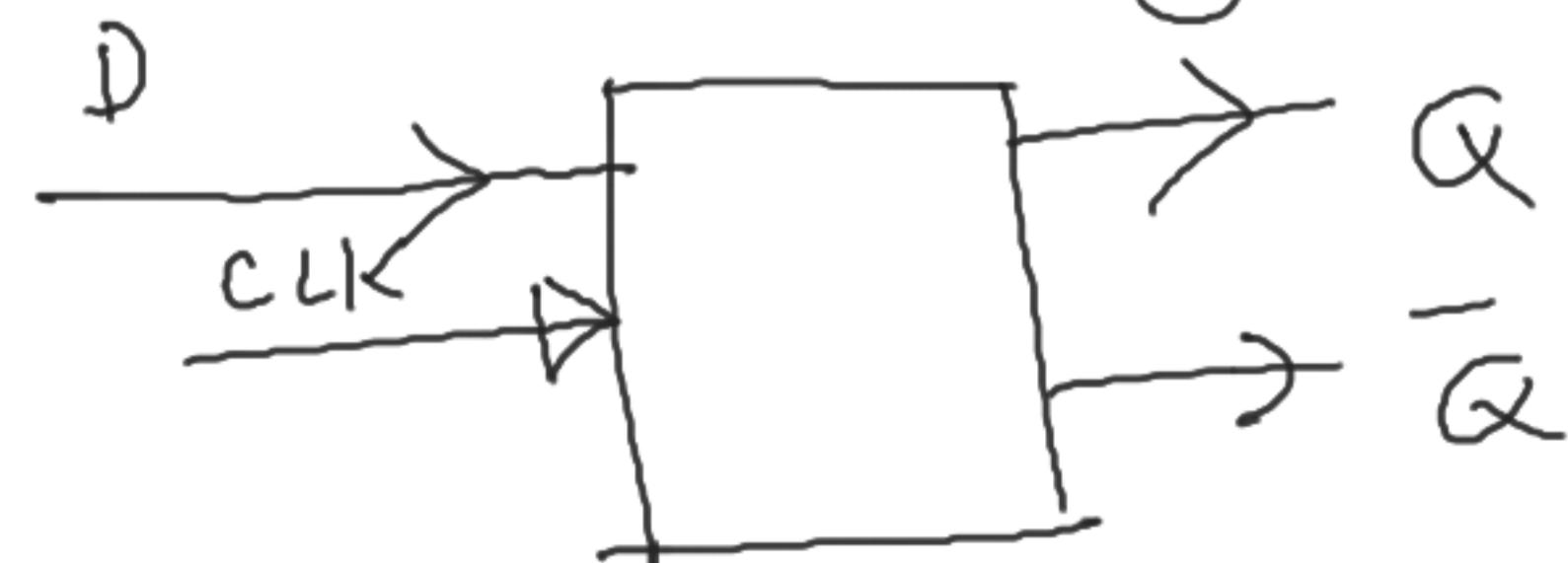

Application of flip flop : Frequency division and counting

MOD 8 UP counter:

f
clock

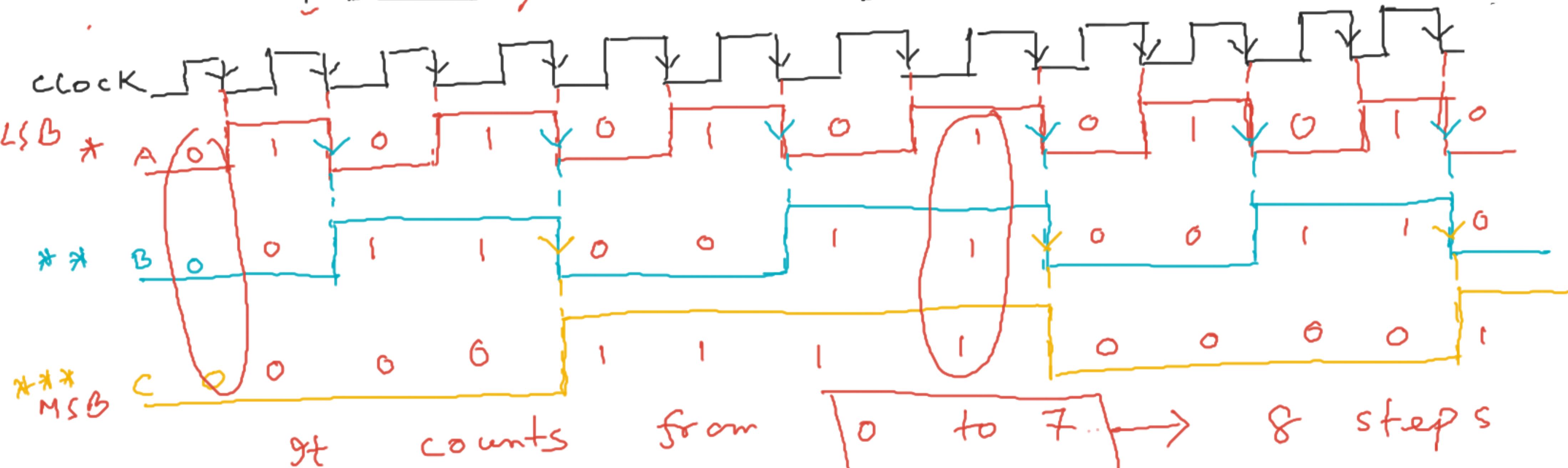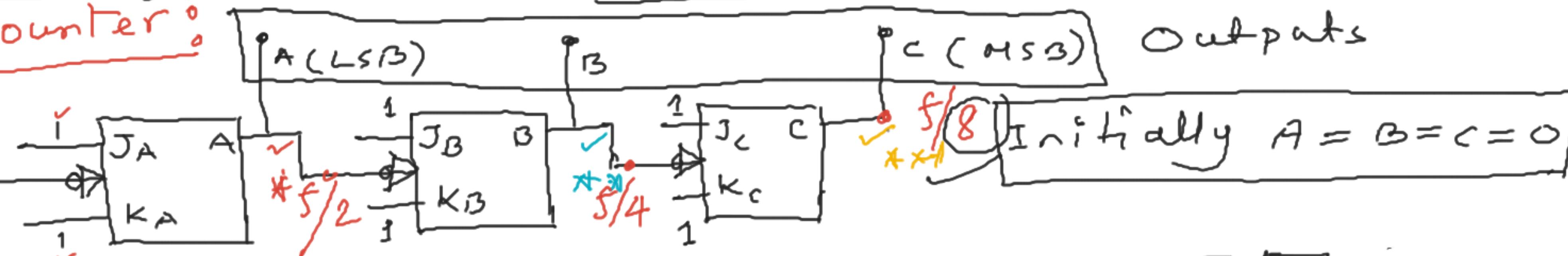

Mod number : Number of
counters is

different steps of the
called mod number.

Number of FF	Mod number
②	$4 = 2^2$
③	$8 = 2^3 \rightarrow 0 \text{ to } 7$
④	$16 = 2^4 \rightarrow 0 \text{ to } 15$
⑤	$32 = 2^5 \rightarrow 0 \text{ to } 31$
⑥	$64 = 2^6$

No. of FF

Mod number = 2
of counter

8 FFs

Input frequency

is 2 MHz.

1) Find mod number.

2) Find output frequency.


1) Mod number = $2^8 = 256$

2) Output frequency = $\frac{2 \times 10^3}{256} = 7.8125 \text{ kHz}$

output frequency = $\frac{\text{Input frequency}}{\text{Mod number}}$

Range of counter = 0 to $(\text{Mod number} - 1)$
 $= 0 \text{ to } (2^{\text{No. of FF}} - 1)$

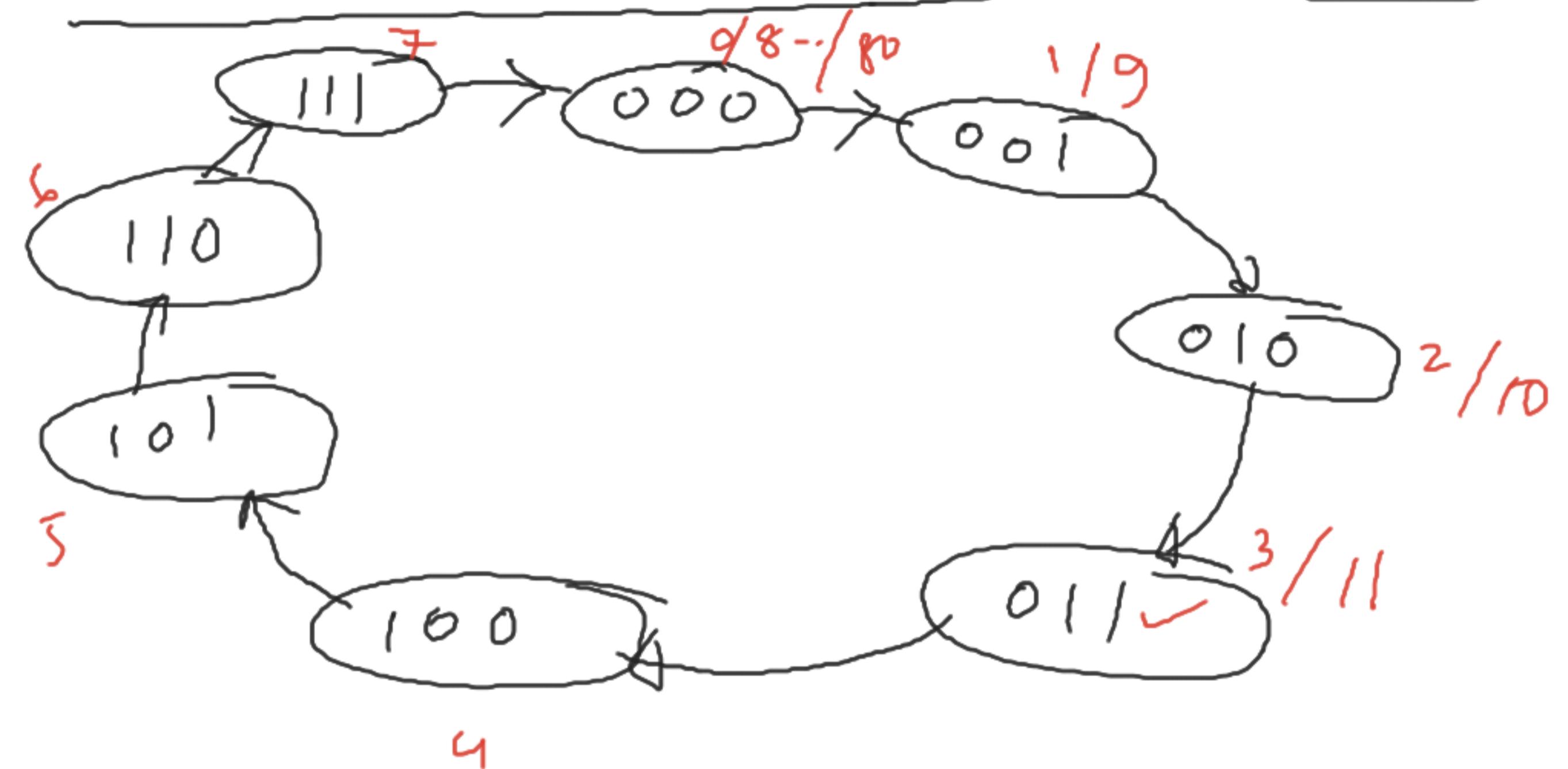Draw the state transition diagram of MOD 8 up counter



Given that initial state of the counter is 000.
Find the counting state after 11 pulses.



→ After 85 pulses
what is the counting states?

$$85 \% 8 = 5$$

$$8 | 85 \quad 10\checkmark$$

80

5

$$5_{10} = 101_2$$

mod
↓

Counting state = (Number of pulses) % (Mod number)

If Initial state is 101 ✓ Find the counting state after 105 pulses ?

$$\Rightarrow 101_2 = 5_{10}$$
$$5 + 105$$
$$= \boxed{110}$$


8) $\begin{array}{r} 110 \\ 8 \end{array} \Big| 13$

$$\begin{array}{r} 8 \\ \hline 30 \\ 24 \\ \hline \cancel{6} \end{array}$$

$$110 \text{ " } . 8 = 6_{10}$$

110

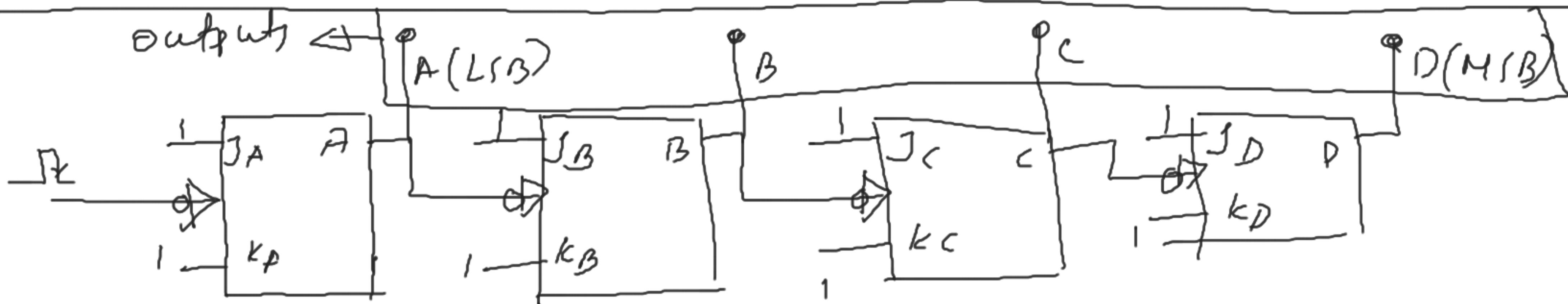Draw the internal circuit of Mod 16 up counter



Initially $A = B = C = D = 0$

- Q 1)
- Mod number = $2^6 = 64$
 - Output frequency = $\frac{1 \times 10^3}{64} = 15.625 \text{ KHz}$
 - 0 to 63
 - $9 + 129 = 138$

$$64 \mid 138 \mid 2$$

001010 ✓


Q 2) 

$$\frac{20 \text{ kHz}}{2} = 10 \text{ kHz}$$

$$\begin{array}{r}
 2^7 \quad 2^6 \quad 2^5 \quad 2^4 \quad 2^3 \quad 2^2 \quad 2^1 \quad 2^0 \\
 128 \quad 64 \quad 32 \quad 16 \quad 8 \quad 4 \quad 2 \quad 1 \\
 \underline{-} \quad \underline{-} \quad \underline{-} \quad \underline{-} \quad \underline{-} \quad \underline{-} \quad \underline{-} \\
 0 \quad 0 \quad 1 \quad 0 \quad 0 \quad 0 \quad 0 \quad 1
 \end{array}$$

Q 3) 0 - 255 Mod number = 256

a) 

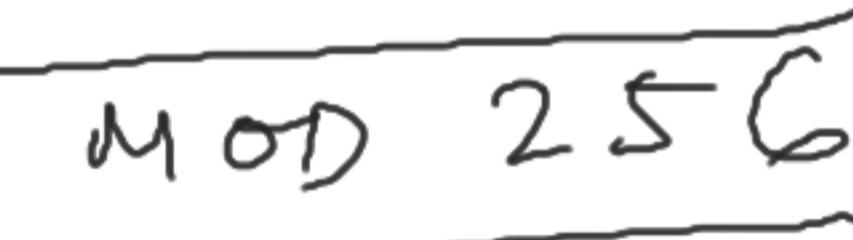b) 

$$2^8 = 256$$

Q 4) a) out frequency = $\frac{512 \text{ kHz}}{2^8} = \frac{512}{256} = 2 \text{ kHz}$

b) $00011001_2 = 2^5 + 5 \cdot 2^0 = 545 / 256$

$256 \left| \begin{matrix} 545 \\ 512 \end{matrix} \right.^2$

$\underline{33}$



$= 33_{10}$