



# University of Asia Pacific

## Admit Card Mid-Term Examination of Fall, 2020

Financial Clearance

PAID

Registration No : 19101020

Student Name : Shawan Das

Program : Bachelor of Science in Computer Science and  
Engineering



SL.NÖ.	CÖURSE CÖDE	CÖURSE TITLE	CÖ.HR.	EXAM. SCHÖDULE
1	CSE 207	Algorithms	3.00	
2	CSE 210	Digital Logic & System Design Lab	1.50	
3	MTH 205	Math IV: Differential Equations and Fourier and Laplace Transformations	3.00	
4	CSE 208	Algorithms Lab	1.50	
5	CSE 209	Digital Logic & System Design	4.00	
6	CSE 211	Database Systems	3.00	
7	CSE 212	Database Systems Lab	1.50	
8	ECN 201	Economics	2.00	

Total Credit: 19.50

1. Examinees are not allowed to enter the examination hall after 30 minutes of commencement of examination for mid semester examinations and 60 minutes for semester final examinations.

2. No examinees shall be allowed to submit their answer scripts before 50% of the allocated time of examination has elapsed.

3. No examinees would be allowed to go to washroom within the first 60 minutes of final examinations.

4. No student will be allowed to carry any books, bags, extra paper or cellular phone or objectionable items/incriminating paper in the examination hall.  
Violators will be subjects to disciplinary action.

This is a system generated Admit Card. No signature is required.

# MID-TERM, Fall- 2020

Name: SHAWAN DAS

ID : 19101020

Dept.: C.S.E.


Year: 2<sup>nd</sup> semester: 2<sup>nd</sup>

Course Title: Digital Logic & System Design.


Course Code:- C.S.E.-209

Date: 23-02-2021

Ans of Q1 (OR part)

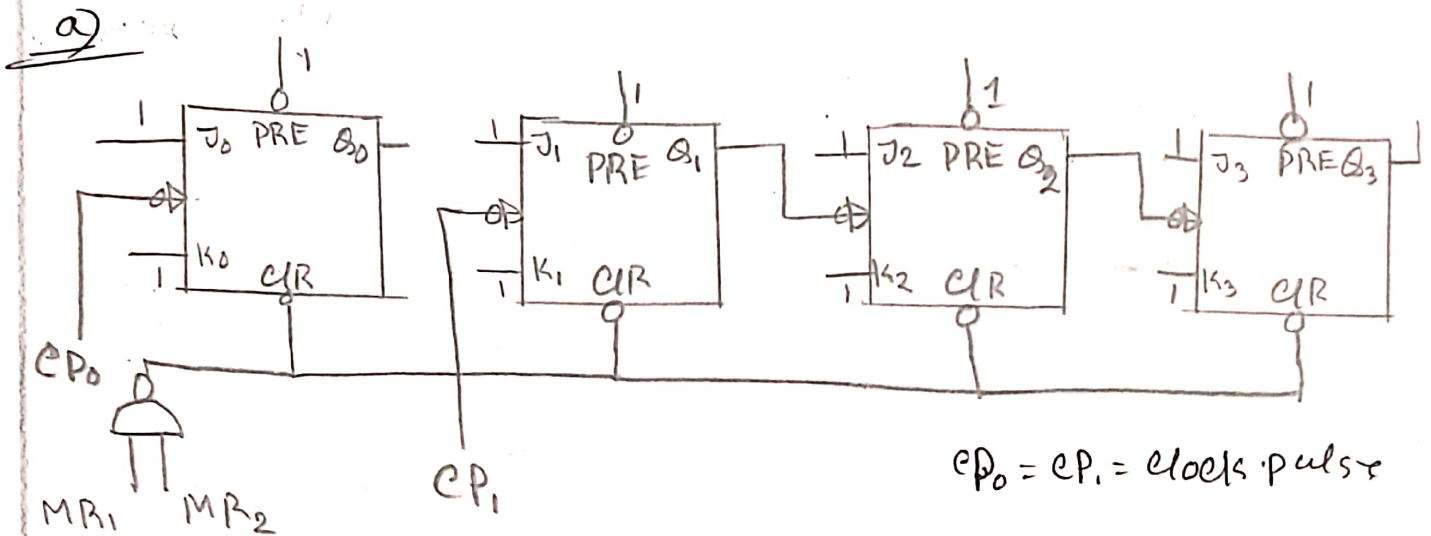


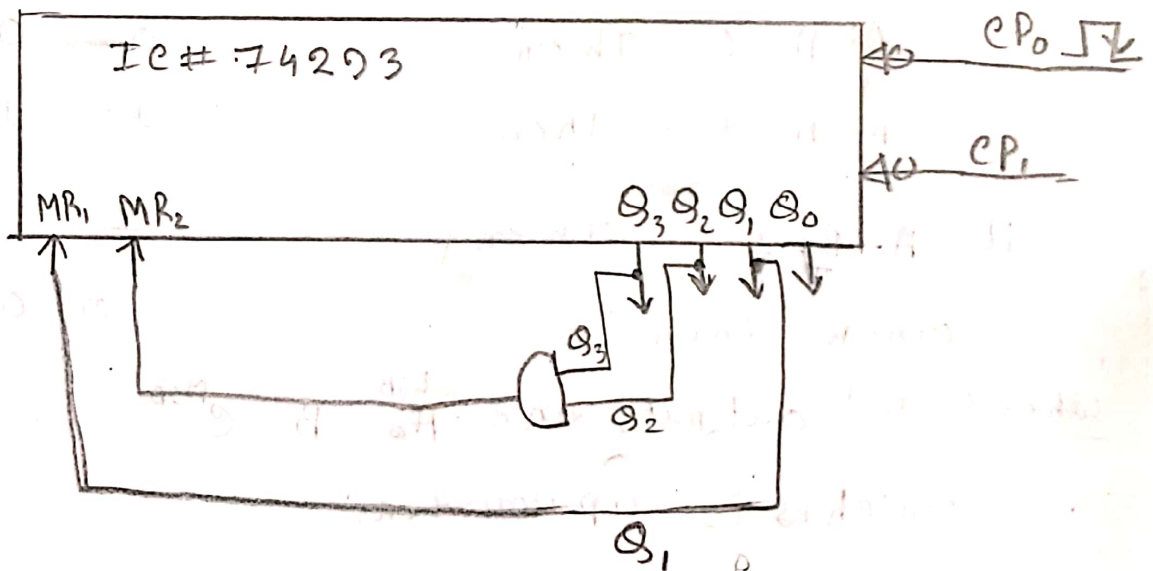- b)
- 13  $\rightarrow$  1101
  - 14  $\rightarrow$  1110  $\rightarrow$  output will be 0. when  $Q_3 = Q_2 = Q_1 = 1$
  - 15  $\rightarrow$  1111  $\rightarrow$  All will be 1  $\rightarrow$  CLR = 0.



counts 0 to 13 (MOD-14)

(c)

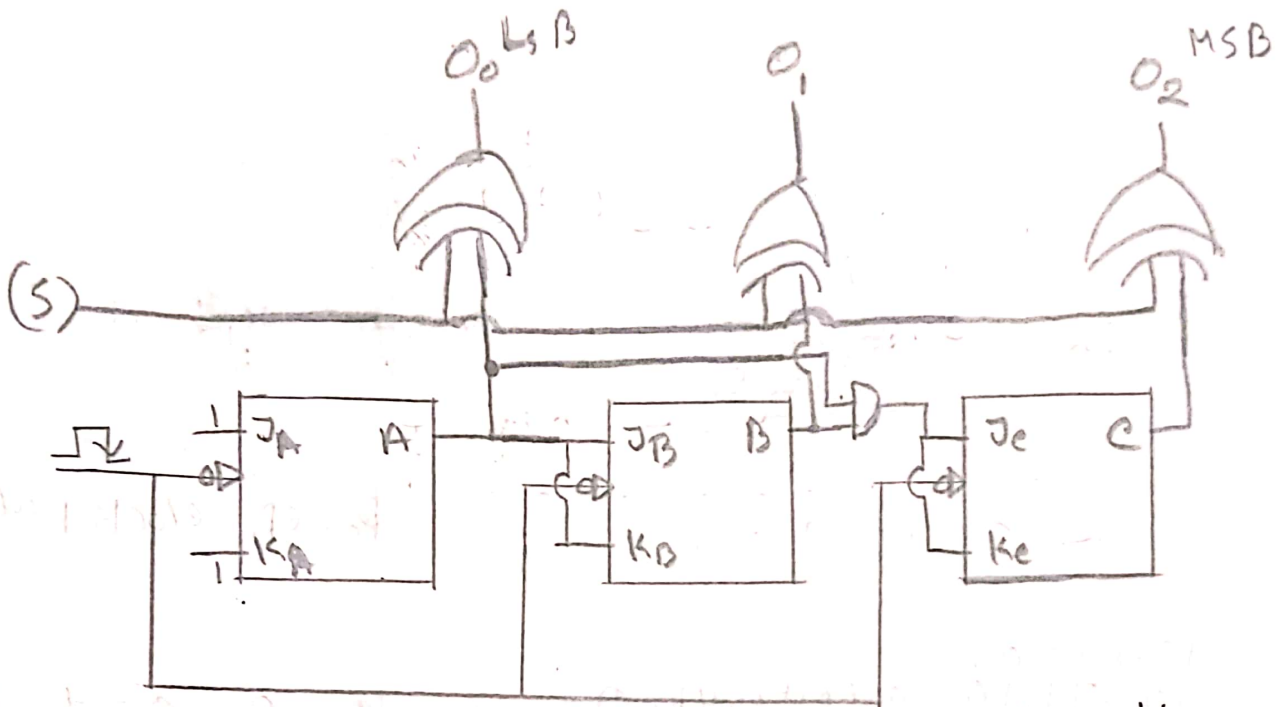

when  $S=0$  A is always toggle so

At  $A=0$  Then

At  $A=1$  Then

if  $A=B=1$  Then

otherwise then

when  $S=0$  outputs are  $A_{LSB} B C_{MSB}$

which is up counter.


when  $S=1$  outputs are  $\overline{A}_{LSB} \overline{B} \overline{C}_{MSB}$

which is down counter.

J	K
1	1
0	0
1	1 ( $J_A = \overline{B}$ )
1	1
0	0

(Any) ob 02


a)

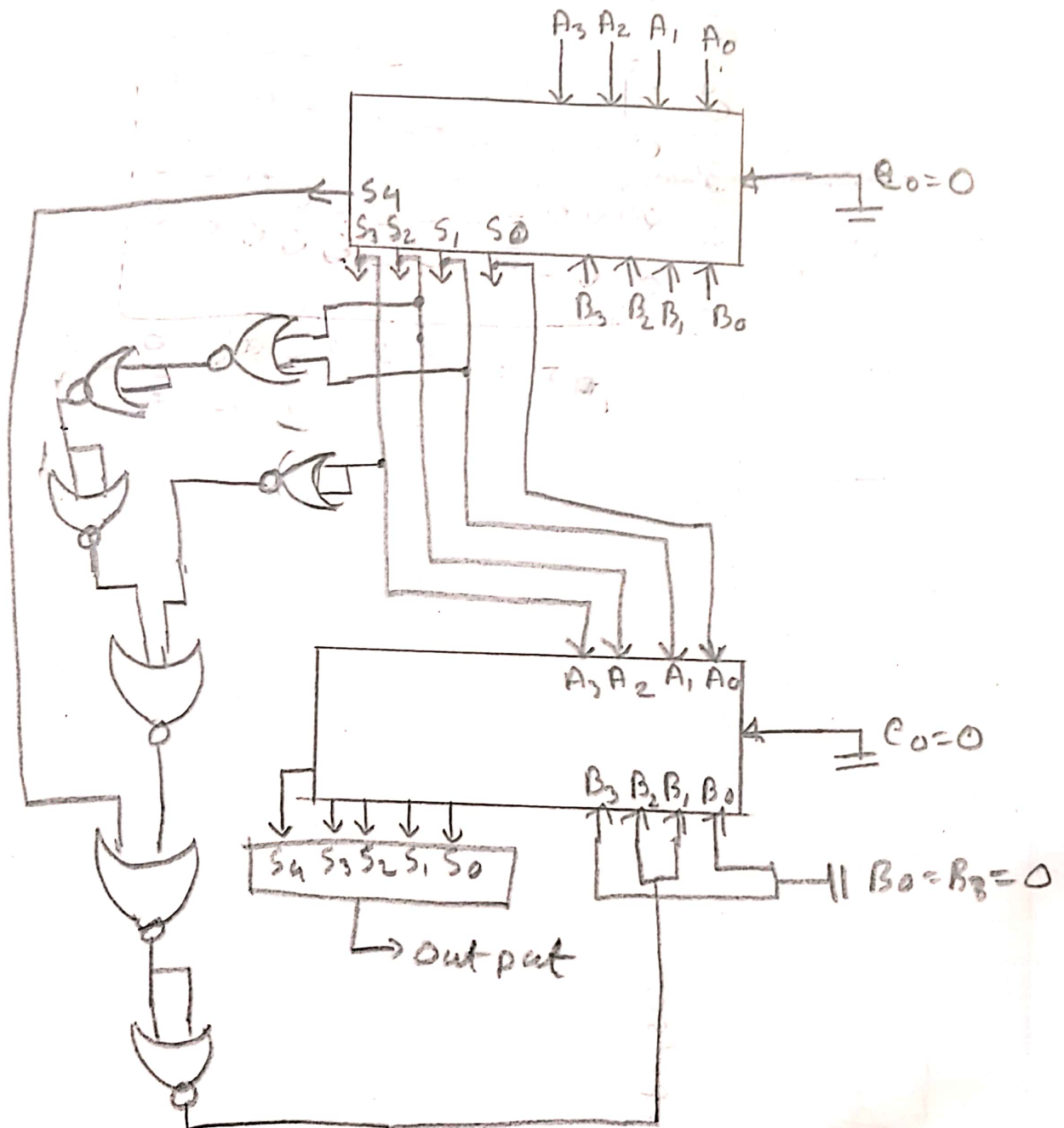

in BED ADDER if  $s_{sum} > 9$  we have to add 10 to Add 8.  
so if  $s_4 = 1$  OR  $s_3 = 1$  AND  $(s_1 = 1 \text{ OR } s_2 = 1)$  Add 0.110



(b)

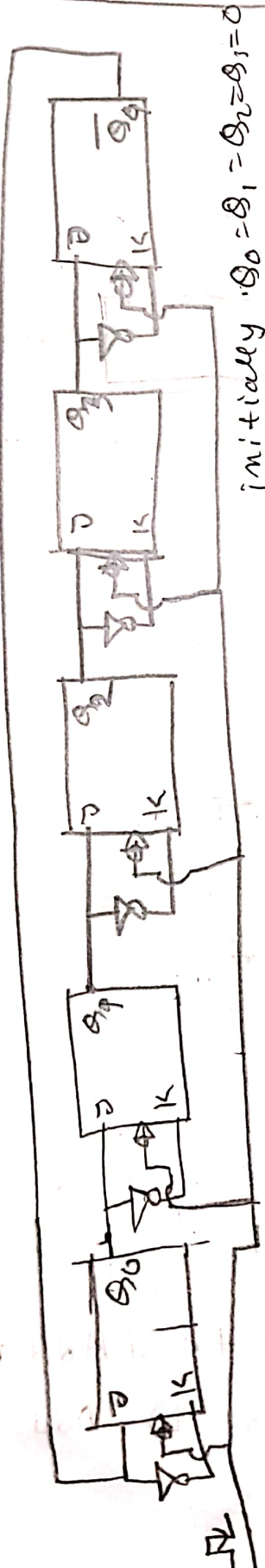

	$Q_4$	$Q_3$	$Q_2$	$Q_1$	$Q_0$
1	0	0	0	0	0
2	1	0	0	0	0
3	1	1	0	0	0
4	1	1	1	0	0
5	1	1	1	1	0
6	0	1	1	1	1
7	0	0	1	1	1
8	0	0	0	1	1
9	0	0	0	0	1
10	0	0	0	0	0

Alternating pulses:

$$Q_0 = Q_4$$

$$Q_1 = Q_0$$

$$Q_2 = Q_1$$

$$Q_3 = Q_2$$

$$Q_4 = Q_3$$

Q. 03 (a)

(i) Number of Flip Flop = 8

$$\therefore \text{MOD number} = 2^8 = 256$$

(ii) input frequency = 16 MHz  
= 16000 KHz

$$\text{output frequency} = \frac{16000 \text{ KHz}}{256} = 62.5 \text{ KHz}$$

(iii) Range: 0 to 255

(iv) 10101000

(b) (i) It happens because the 7 bit <sup>counter</sup> can count from 0 to 127. After 127 it will start counting from 0.

(ii) He can use upto 8 bit counter. such as if he uses 10 bit counter it will count from 0 to 1023.

② ①

A	B	C	D	X
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	1	1

	$\overline{A}B$	$A\overline{B}$	$AB$	$\overline{A}\overline{B}$
$\overline{C}D$	1	.	1	.
$C\overline{D}$	1	.	1	.
$CD$	1	1	1	1
$\overline{C}D$	1	.	1	.

$$X = \overline{C}D + \overline{A}B + AB$$

$$= \overline{C}D + \overline{A \oplus B}$$

